

Physics 2135 Exam 2

October 20, 2015

Exam Total

200 / 200


Printed Name: _____ **Key** _____

Rec. Sec. Letter: N/A

Five multiple choice questions, 8 points each. Choose the **best** or **most nearly correct** answer.


B 1. A straight wire segment carries a current I . The wire segment is in a region where there is a uniform magnetic field B as shown. What is the direction of the magnetic force on the wire segment?

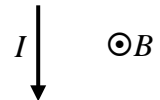- [A] \otimes [B] \leftarrow
[C] \rightarrow [D] \odot




A 2. Three identical light bulbs are connected to a battery as shown in the figure to the right. Which light bulb will dissipate the most power?

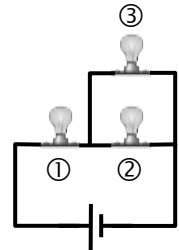- [A] bulb ① [B] bulb ②
[C] bulb ③ [D] all three bulbs will dissipate the same power



B 3. A circular current loop has an area of $A = 200 \text{ cm}^2$ and is oriented so that the plane of the loop is parallel to a constant magnetic field $B = 0.6 \text{ T}$. The magnitude of the torque acting on the current loop is $0.024 \text{ m}\cdot\text{N}$. What is the current I in the loop?

- [A] 1 A [B] 2 A
[C] 4 A [D] 0 A

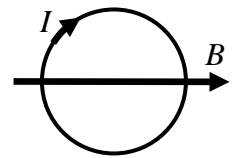


C 4. A charged particle moves through a region of space that has both a uniform electric field and a uniform magnetic field. In order for the particle to move through this region at a constant velocity,

- [A] the electric and magnetic fields must point in the same direction
[B] the electric and magnetic fields must point in opposite directions
[C] the electric and magnetic fields must point in perpendicular directions
[D] the answer depends on the sign of the particle's electric charge.

ABCD 5. When will I get a picture of a levitating dog on my Physics 2135 exam?

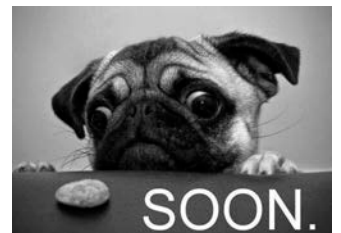- [A] soon [B] exam 3
[C] ask Dr. Parris [D] the answer is always magnetism



6. (40 points total) An air-filled parallel-plate capacitor consists of two square plates of length L and plate separation d . It is charged to an initial voltage V_0 .

(a) (10 points) Calculate the energy U_0 stored in the capacitor in terms of L , d , V_0 , and constants.

$$C_0 = \frac{\epsilon_0 A}{d} = \frac{\epsilon_0 L^2}{d} \quad k=1 \text{ for air}$$

$$U_0 = \frac{1}{2} C_0 V_0^2 = \frac{1}{2} \left(\frac{\epsilon_0 L^2}{d} \right) V_0^2 = \boxed{\frac{\epsilon_0 L^2 V_0^2}{2d}}$$

(b) (20 points) The capacitor is disconnected from the voltage source. After that, an insulator having a dielectric constant $\kappa > 1$ is inserted between the plates of the capacitor. The dielectric material fills the space between the plates. Find the energy U_1 stored in the capacitor after the dielectric is inserted. Express your answer in terms of L , d , V_0 , κ , and constants.

$$Q_1 = Q_0 \text{ (disconnected)} \quad C_1 = \frac{\kappa \epsilon_0 A}{d} = \frac{\kappa \epsilon_0 L^2}{d} = \kappa C_0$$

$$U_1 = \frac{Q_1^2}{2C_1} = \frac{Q_0^2}{2C_1} = \frac{C_0^2 V_0^2}{2C_1} = \frac{C_0^2 V_0^2}{2\kappa C_0} = \frac{C_0 V_0^2}{2\kappa}$$

$$U_1 = \frac{\left(\frac{\epsilon_0 L^2}{d} \right) V_0^2}{2\kappa} = \boxed{\frac{\epsilon_0 L^2 V_0^2}{2\kappa d}}$$

(c) (10 points) The potential difference V_1 between the capacitor plates after the dielectric has been inserted is (circle one below)


less than V_0

equal to V_0

greater than V_0

7. (40 points total) Consider the circuit shown. The **terminal voltage** of the battery is $V_{ab}=120\text{ V}$.

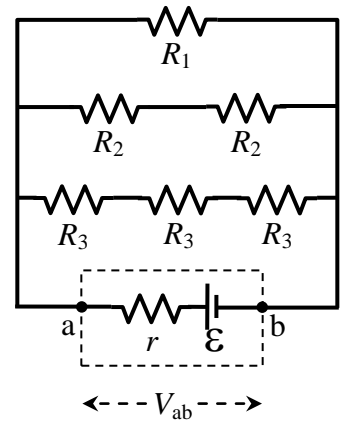(a) (20 points) Each resistor dissipates 100W. Calculate R_1 , R_2 , and R_3 . Clearly indicate any OSEs you use.



R_1 branch: $R_{eq} = R_1 \Rightarrow V_1 = V_{ab}$

R_2 branch: $R_{eq} = 2R_2 \Rightarrow V_2 = V_{ab}/2$

R_3 branch: $R_{eq} = 3R_3 \Rightarrow V_3 = V_{ab}/3$

$P = \frac{V^2}{R} \Rightarrow R = \frac{V^2}{P}$

$R_1 = \frac{120^2}{100} = 144\ \Omega$

$R_2 = \frac{60^2}{100} = 36\ \Omega$

$R_3 = \frac{40^2}{100} = 16\ \Omega$

(b) (10 points) If the battery has an internal resistance of $r = 0.8\ \Omega$, what is its emf?

method 1: use $I = V/R$ & $V_{ab} = \mathcal{E} - Ir$

$I_1 = \frac{120}{144} = \frac{10}{12}$

$I_2 = \frac{120}{36+36} = \frac{10}{6}$

$I_3 = \frac{120}{3(16)} = \frac{10}{4}$


$I_{total} = I_1 + I_2 + I_3 = \frac{10+20+30}{12} = 5\text{ A}$

$\mathcal{E} = V_{ab} + I_{total} r = 120 + 5(0.8) = 124\text{ V}$

method 2: calculate R_{eq} of R_1 , R_2 's & R_3 's

$\frac{1}{R_{P's}} = \frac{1}{144} + \frac{1}{72} + \frac{1}{48} = \frac{6}{144}$

$R_{P's} = 24\ \Omega$

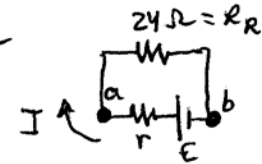

$V_{ab} = 120\text{ V} \Rightarrow I = \frac{120}{24} = 5\text{ A}$

$\mathcal{E} = V_{ab} + Ir = 124\text{ V}$


(c) (10 points) A non-ideal ammeter is connected to measure the current passing through R_1 . How does the power dissipated in R_1 change? (Circle one of the answers below.)

increases

does not change

decreases

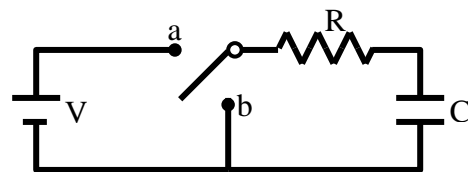8. (40 points total) In the circuit shown, $R = 50 \text{ k}\Omega$, $V = 25 \text{ volts}$, and $C = 10 \text{ }\mu\text{F}$. The capacitor is initially uncharged.



(a) (10 points) What is the initial current through the resistor immediately after the switch is set to position a?

$$\text{Initially } V - V_R - V_C = 0 \Rightarrow V_R = IR = V$$

$$\text{OK to just start here} \rightarrow I = \frac{V}{R} = \frac{25}{50,000} = \boxed{0.5 \text{ mA}}$$

you can also take $I = \frac{dq}{dt}$ and get same result

(b) (20 points) What is the voltage across the capacitor 1 second after the switch is set to a?

$$Q(t) = Q_f(1 - e^{-t/RC})$$

$$RC = (50 \times 10^3)(10 \times 10^{-6}) = 0.5 \text{ s}$$

$$CV(t) = C V(1 - e^{-t/RC})$$

$$V(t) = V(1 - e^{-t/RC})$$

$$V(1) = 25(1 - e^{-1/0.5}) = 25(1 - 0.135) = \boxed{21.6 \text{ V}}$$

(c) (10 points) The capacitor is allowed to fully charge. The switch is then set to position b. How much time elapses after the switch is set to position b until the charge stored in the capacitor is equal to one-fourth of its fully-charged value?

$$Q(t) = Q_0 e^{-t/RC}$$


$$\frac{1}{4} Q_0 = Q_0 e^{-t/RC}$$

$$\frac{1}{4} = e^{-t/RC}$$

$$-\frac{t}{RC} = \ln \frac{1}{4}$$

$$t = -RC \ln\left(\frac{1}{4}\right) = -0.5 \ln \frac{1}{4} = \boxed{0.693 \text{ s}}$$

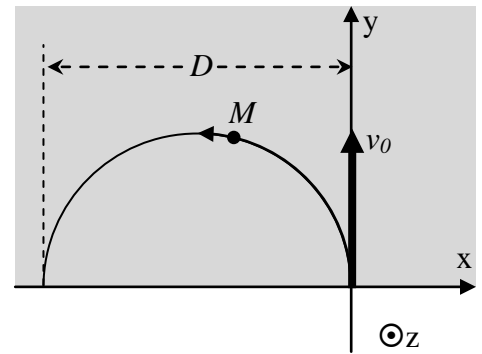9. (40 points total) A particle of mass M and positive charge Q enters a region (indicated by the shaded area) of uniform magnetic field, moving initially with a velocity $\vec{v} = v_0 \hat{j}$. The particle moves in a circular path in the xy -plane and crosses the x -axis at $x = -D$.



(a) (5 points) What is the direction of the magnetic field?

Circle one: $+\hat{k}$ $-\hat{k}$ $+\hat{i}$ $-\hat{i}$


(b) (20 points) Begin with starting equations and calculate the magnitude of the magnetic field. Express your answer in terms of parameters given in the statement of the problem.

$$\vec{F} = Q\vec{v} \times \vec{B} = M\vec{a} \quad \text{with } \vec{v} \perp \vec{B}$$

$$Qv_0 B = \frac{Mv_0^2}{r} = \frac{Mv_0^2}{D/2} = \frac{2Mv_0^2}{D}$$

$$B = \frac{2Mv_0}{QD}$$

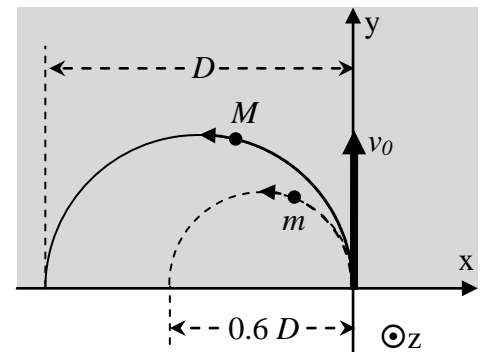(c) (15 points) A second particle of unknown mass having the same charge Q and the same initial velocity $v_0 \hat{j}$ moves in a circular path in the magnetic field region and crosses the x -axis at $x = -0.6D$. Begin with starting equations or an equation you derived in part (b), and calculate the mass of the second particle. Express your answer in terms of M .



$$\text{from part b } QB = \frac{mv_0}{r} \Rightarrow m = \frac{QrB}{v_0}$$

$$m = \frac{Q \frac{1}{2} (0.6D) B}{v_0} = 0.6 \frac{QDB}{2v_0} = \boxed{0.6 M}$$