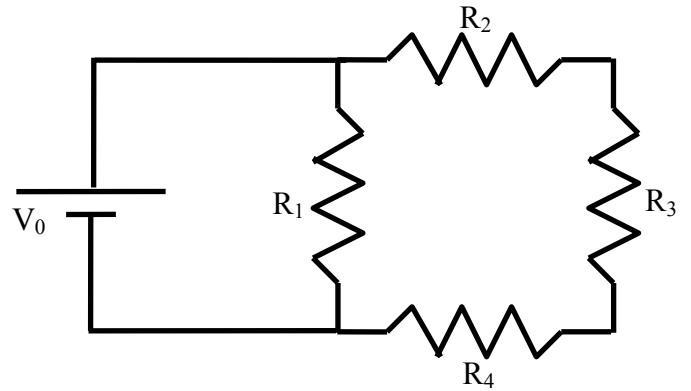


6. Wire A has length L and wire B has length $2L$. Both wires have circular cross-sections. At room temperature (20°C) both wires have the same resistance. Wire A is made from material that has a resistivity that is one-half that of the material used to make wire B.

(20) a) Find the ratio of the radii of the two wires r_B/r_A .


(20) b) Both wires are now heated to 520°C . What is the ratio of the resistances of the two wires R_B/R_A at this elevated temperature? The temperature coefficient of the material for wire A is $2\text{ }(^{\circ}\text{C})^{-1}$, and for the material in wire B it is $5\text{ }(^{\circ}\text{C})^{-1}$. You may assume that the wires do not expand upon heating.

7. For the resistor circuit shown $R_1 = 6.0 \Omega$, $R_2 = 1.0 \Omega$, $R_3 = 2.0 \Omega$, and $R_4 = 3.0 \Omega$.
(20) a) Find the equivalent resistance.



- (20) b) The power supply provides a potential difference $V_0 = 18 \text{ V}$. Determine the power dissipated by resistor R_4 .

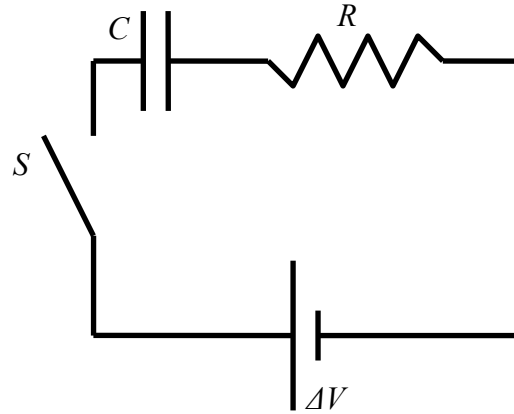8. For the circuit shown $C = 6 \mu\text{F}$ and $\Delta V = 25 \text{ V}$. Initially the capacitor is uncharged. The switch S is then closed and the capacitor begins to charge.
- (10) a) Determine the charge on the capacitor a very long time ($t \rightarrow \infty$) after the switch is closed.



- (30) b) After the switch has been closed for time T the voltage across the capacitor is found to be $1/5$ of its final value. Find R ? You should express your answer in terms of system parameters (do not attempt a numerical solution).

