

Name: \_\_\_\_\_ Section: \_\_\_\_\_


For questions 1-5, select the best answer. For problems 6-9, solutions must begin with an Official Starting Equation, when appropriate. Work must be shown to receive credit. Calculators are not allowed.

- (8) \_\_\_\_\_ 1. Two light bulbs are both rated for 110V operation. One bulb is 100W and the other is 40W. They are wired in parallel with a 110V source. The 100W bulb burns out. What happens next?
- [A] The current flowing through the 40W bulb goes to zero.  
 [B] The voltage across the 40W bulb decreases but does not decrease to zero.  
 [C] The current flowing through the 40W bulb increases to  $10/4$  of its initial value.  
 [D] None of the above.





- (8) \_\_\_\_\_ 2. The diagram shows a side view of four loops in a uniform magnetic field. All four loops are identical. For which loop is the potential energy of the magnetic dipole equal to zero?

[A] ①  
 [C] ③

[B] ②  
 [D] ④

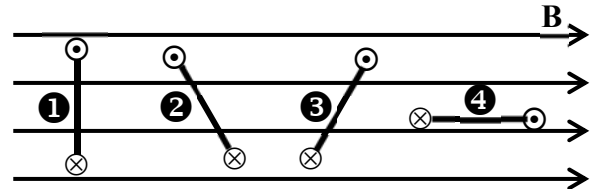

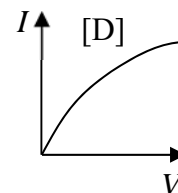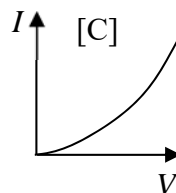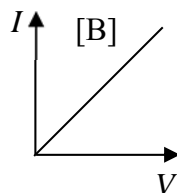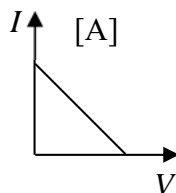
- (8) \_\_\_\_\_ 3. A resistor with resistance  $R$  obeys Ohm's law. It is connected to a variable voltage source and the current through the resistor as a function of applied voltage is measured. Which plot (A, B, C, or D) best describes the results of the measurements?



- (8) \_\_\_\_\_ 4. A vertical straight wire of length  $L$ , carries a current  $I$  upward from the ground. The earth's magnetic field, which is directed towards the north, exerts a force on the wire. The direction of the force on the wire is towards the
- [A] north      [B] south      [C] east      [D] west.


- (8) \_\_\_\_\_ 5. Free point problems often involve animals because
- [A] they are found in fields.  
 [B] we lack resistance against them.  
 [C] they have the capacity to charge.  
 [D] of unknown reasons, the subject of current research.

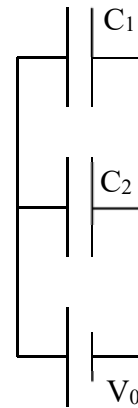6. Two capacitors with capacitance  $C_1 = C$  and  $C_2 = 2C$  are connected across a potential difference  $V_0$  as shown. **Express answers in terms of given quantities. Simplify when possible.**



- (10) (a) Calculate the charge on each capacitor.

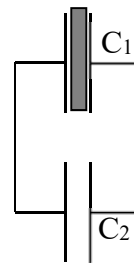- (10) (b) After the *battery is disconnected*, a dielectric with dielectric constant  $K = 4$  is inserted into capacitor  $C_1$  completely filling the space between the capacitor plates. Calculate the charge on each capacitor now.




7. A light bulb has a resistance of  $20 \Omega$  when off ( $20^\circ\text{C}$ ) and a resistance of  $120 \Omega$  when on (hot).

- (20) If the temperature coefficient for the light bulb filament is  $1/60 (\text{C}^\circ)^{-1}$  what is the operating temperature of the bulb? You may neglect thermal expansion of the filament. **A numerical answer is required.**

8. Numerical answers are required for all parts of problem 8.

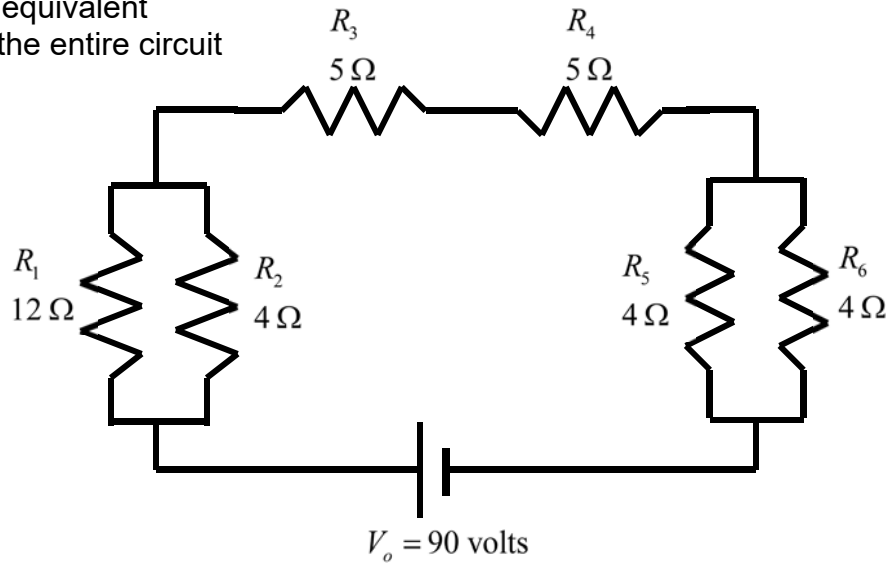- (10) (a) Calculate the equivalent resistance of the entire circuit shown.




- (10) (b) Find the current  $I_3$  in resistor  $R_3$ .

- (10) (c) Find the voltage  $V_1$  across resistor  $R_1$ .

- (10) (d) Assume resistor  $R_5$  has a cylindrical shape with a diameter of 6 mm, a length  $\ell$  and is made out of Carbon. Estimate the length  $\ell$  of the Carbon rod so that it has a resistance of  $4\ \Omega$ . The resistivity of Carbon  $\rho = 3.6 \times 10^{-5}\ \Omega \cdot m$  and assume  $\pi \approx 3$  for estimation purposes. **A numerical answer of one significant figure is required.**

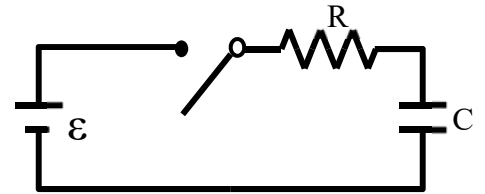
9. In the circuit shown, an uncharged capacitor with capacitance  $C$  and a resistor with resistance  $R$  are in series with a battery of emf  $\mathcal{E}$ .



- (10) (a) After the switch has been closed for a very long time what is the final charge on the capacitor and what is the total energy stored in it? **Express your answers in terms of  $\mathcal{E}$  and  $C$ .**
- (15) (b) When the power dissipated by the resistor is equal to  $\mathcal{E}^2/(9R)$ , what is the energy stored in the capacitor? **Express your answer in terms of  $\mathcal{E}$  and  $C$ .**
- (15) (c) Determine the time after the switch is closed when the charge on the capacitor is  $\frac{2}{3}$  of its final charge. **Express your answers using  $\mathcal{E}$ ,  $C$ , and  $R$ , as appropriate.**

10. An electron of mass  $m_e$  and charge  $-e$  enters a region (indicated by the shaded area) of uniform magnetic field, moving initially with a velocity  $v = v_0$  along positive  $y$ -axis. The electron moves in a circular path in the  $xy$ -plane and crosses the  $x$ -axis at  $x = -D$ . Express all answers for problem 10 in terms of parameters given in the statement of the problem.

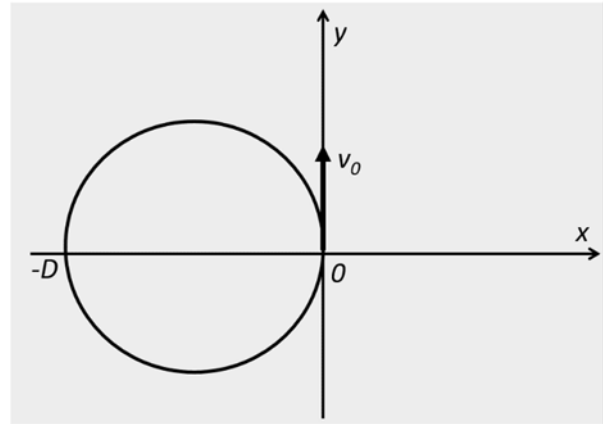- (15) (a) Begin with starting equations and calculate the magnitude of the magnetic field.



- (5) (b) Which of the following is the direction of the magnetic field? [Circle the correct answer.]
- |                |                |                |                      |
|----------------|----------------|----------------|----------------------|
| [A] $\hat{i}$  | [B] $\hat{j}$  | [C] $\hat{k}$  | [D] Clockwise        |
| [E] $-\hat{i}$ | [F] $-\hat{j}$ | [G] $-\hat{k}$ | [H] Counterclockwise |
- (10) (c) Calculate the magnitude of the magnetic flux through the area defined by the circular path.

- (10) (d) A positron (particle of mass  $m_e$  and charge  $+e$ ) enters the same region with the same initial velocity  $v = v_0$  along the positive  $y$ -axis. Find the position where the positron crosses the  $x$ -axis in its circular path.