

Name: _____ Section: _____


For questions 1-5, select the best answer. For problems 6-9, solutions must begin with an Official Starting Equation, when appropriate. Work must be shown to receive credit. Calculators are not allowed.

- (8) D 1. Two light bulbs are both rated for 110V operation. One bulb is 100W and the other is 40W. They are wired in parallel with a 110V source. The 100W bulb burns out. What happens next?
 [A] The current flowing through the 40W bulb goes to zero.
 [B] The voltage across the 40W bulb decreases but does not decrease to zero.
 [C] The current flowing through the 40W bulb increases to 10/4 of its initial value.
 [D] None of the above.





- (8) D 2. The diagram shows a side view of four loops in a uniform magnetic field. All four loops are identical. For which loop is the potential energy of the magnetic dipole equal to zero?

[A] ①
 [C] ③

[B] ②
 [D] ④

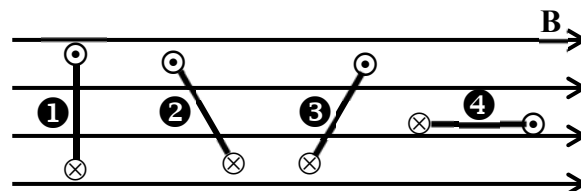

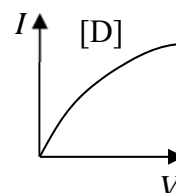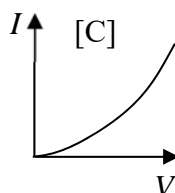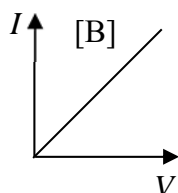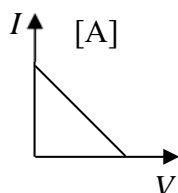
- (8) B 3. A resistor with resistance R obeys Ohm's law. It is connected to a variable voltage source and the current through the resistor as a function of applied voltage is measured. Which plot (A, B, C, or D) best describes the results of the measurements?



- (8) D 4. A vertical straight wire of length L , carries a current I upward from the ground. The earth's magnetic field, which is directed towards the north, exerts a force on the wire. The direction of the force on the wire is towards the
 [A] north [B] south [C] east [D] west.

- (8) _____ 5. Free point problems often involve animals because
 [A] they are found in fields.
 [B] we lack resistance against them.
 [C] they have the capacity to charge.
 [D] of unknown reasons, the subject of current research.

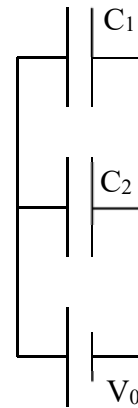6. Two capacitors with capacitance $C_1 = C$ and $C_2 = 2C$ are connected across a potential difference V_0 as shown. **Express answers in terms of given quantities. Simplify when possible.**




- (10) (a) Calculate the charge on each capacitor.

$$C = \frac{Q}{V} \quad Q_1 = C_1 V_1 \quad Q_2 = C_2 V_2$$

$$\boxed{Q_1 = CV_0} \quad \boxed{Q_2 = 2CV_0}$$

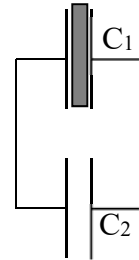- (10) (b) After the *battery is disconnected*, a dielectric with dielectric constant $K = 4$ is inserted into capacitor C_1 completely filling the space between the capacitor plates. Calculate the charge on each capacitor now.



$$C_{1f} = \kappa C_1 \quad Q_{T0} = Q_{Tf} \quad Q_{1f} = C_{1f} V_f$$

$$C_{1f} = 4C \quad CV_0 + 2CV_0 = C_{1f} V_f + C_2 V_f \quad Q_{1f} = 4C \left(\frac{1}{2} V_0\right)$$

$$3CV_0 = (4C + 2C) V_f \quad \boxed{Q_{1f} = 2CV_0}$$

$$\frac{3CV_0}{6C} = V_f \quad Q_{2f} = C_2 V_f$$

$$\frac{1}{2} V_0 = V_f \quad Q_{2f} = 2C \left(\frac{1}{2} V_0\right)$$

$$\boxed{Q_{2f} = CV_0}$$

7. A light bulb has a resistance of 20Ω when off (20°C) and a resistance of 120Ω when on (hot).

- (20) If the temperature coefficient for the light bulb filament is $1/60 (\text{C}^{-1})$ what is the operating temperature of the bulb? You may neglect thermal expansion of the filament. **A numerical answer is required.**

$$R = \rho \frac{L}{A} \quad \frac{\frac{120\Omega}{20\Omega} - 1}{1/(60^\circ\text{C})} + 20^\circ\text{C} = T$$

$$R = \rho_0 \frac{L}{A} [1 + \alpha(T - T_0)]$$

$$R = R_0 [1 + \alpha(T - T_0)] \quad \frac{6-1}{1/(60^\circ\text{C})} + 20^\circ\text{C} = T$$

$$\frac{R}{R_0} = 1 + \alpha(T - T_0) \quad 5(60^\circ\text{C}) + 20^\circ\text{C} = T$$

$$\frac{R}{R_0} - 1 = \alpha(T - T_0) \quad 300^\circ\text{C} + 20^\circ\text{C} = T$$

$$\frac{\frac{R}{R_0} - 1}{\alpha} = T - T_0 \quad 300^\circ\text{C} + 20^\circ\text{C} = T$$

$$\frac{\frac{R}{R_0} - 1}{\alpha} + T_0 = T \quad \boxed{320^\circ\text{C} = T}$$

/40

8. Numerical answers are required for all parts of problem 8.


- (10) (a) Calculate the equivalent resistance of the entire circuit shown.

$$R_{12} = \left(\frac{1}{12\Omega} + \frac{1}{4\Omega} \right)^{-1} = 3\Omega$$

$$R_{56} = \left(\frac{1}{4\Omega} + \frac{1}{4\Omega} \right)^{-1} = 2\Omega$$

$$R_T = 3\Omega + 5\Omega + 5\Omega + 2\Omega$$

$$R_T = 15\Omega$$

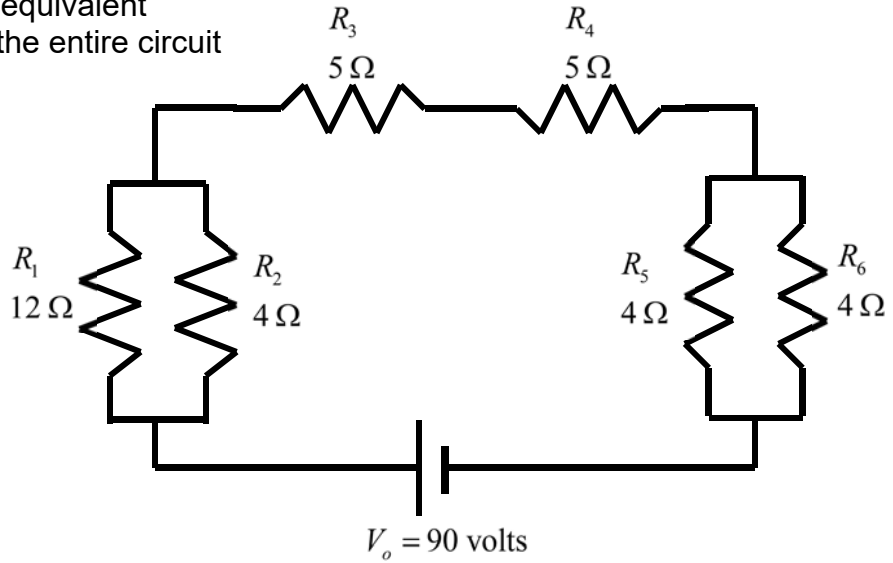

- (10) (b) Find the current I_3 in resistor R_3 .

$$I_3 = I_T = \frac{V_T}{R_T} = \frac{90V}{15\Omega}$$

$$I_3 = 6A$$

- (10) (c) Find the voltage V_1 across resistor R_1 .

$$V_1 = V_{12} = I_{12}R_{12} = I_T R_{12} = (6A)(3\Omega)$$

$$V_1 = 18V$$

- (10) (d) Assume resistor R_5 has a cylindrical shape with a diameter of 6 mm, a length ℓ and is made out of Carbon. Estimate the length ℓ of the Carbon rod so that it has a resistance of 4Ω . The resistivity of Carbon $\rho = 3.6 \times 10^{-5} \Omega \cdot m$ and assume $\pi \approx 3$ for estimation purposes. **A numerical answer of one significant figure is required.**

$$R = \rho \frac{l}{A}$$


$$\frac{RA}{\rho} = l$$

$$\frac{R\pi r^2}{\rho} = l$$

$$\frac{(4\Omega)3(3 \times 10^{-3}m)^2}{3.6 \times 10^{-5}\Omega m} = l$$

$$3m = l$$

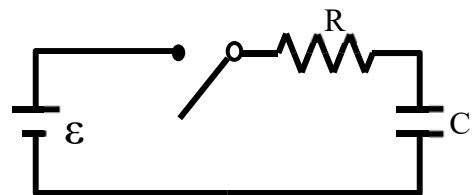9. In the circuit shown, an uncharged capacitor with capacitance C and a resistor with resistance R are in series with a battery of emf \mathcal{E} .



- (10) (a) After the switch has been closed for a very long time what is the final charge on the capacitor and what is the total energy stored in it? **Express your answers in terms of \mathcal{E} and C .**

$$C = \frac{Q}{V}$$

$$Q_f = CV_f$$

$$\boxed{Q_f = C\mathcal{E}}$$

$$U = \frac{1}{2}QV$$

$$U_f = \frac{1}{2}Q_fV_f$$

$$\boxed{U_f = \frac{1}{2}C\mathcal{E}^2}$$

- (15) (b) When the power dissipated by the resistor is equal to $\mathcal{E}^2/(9R)$, what is the energy stored in the capacitor? **Express your answer in terms of \mathcal{E} and C .**

$$P = \frac{V_R^2}{R} = \frac{\mathcal{E}^2}{9R}$$

$$V_R = \frac{\mathcal{E}}{3}$$

$$\mathcal{E} - V_R - V_C = 0$$

$$\mathcal{E} - \frac{\mathcal{E}}{3} = V_C$$

$$\frac{2}{3}\mathcal{E} = V_C$$

$$U = \frac{1}{2}CV^2$$

$$U = \frac{1}{2}C\left(\frac{2}{3}\mathcal{E}\right)^2$$

$$\boxed{U = \frac{2}{9}C\mathcal{E}^2}$$

- (15) (c) Determine the time after the switch is closed when the charge on the capacitor is $\frac{2}{3}$ of its final charge. **Express your answers using \mathcal{E} , C , and R , as appropriate.**

$$Q = Q_f(1 - e^{-t/\tau})$$

$$\frac{2}{3}Q_f = Q_f(1 - e^{-t/RC})$$

$$\frac{2}{3} = 1 - e^{-t/RC}$$

$$e^{-t/RC} = \frac{1}{3}$$

$$-\frac{t}{RC} = \ln\left(\frac{1}{3}\right)$$

$$\boxed{t = -RC \ln\left(\frac{1}{3}\right)} \quad \text{or} \quad \boxed{t = RC \ln(3)}$$

10. An electron of mass m_e and charge $-e$ enters a region (indicated by the shaded area) of uniform magnetic field, moving initially with a velocity $v = v_0$ along positive y -axis. The electron moves in a circular path in the xy -plane and crosses the x -axis at $x = -D$. Express all answers for problem 10 in terms of parameters given in the statement of the problem.


- (15) (a) Begin with starting equations and calculate the magnitude of the magnetic field.

$$\vec{F} = q(\vec{E} + \vec{v} \times \vec{B})$$

$$|qvB| = \frac{mv^2}{r}$$

$$r = \frac{D}{2}$$

$$B = \frac{2m_e v_0}{eD}$$

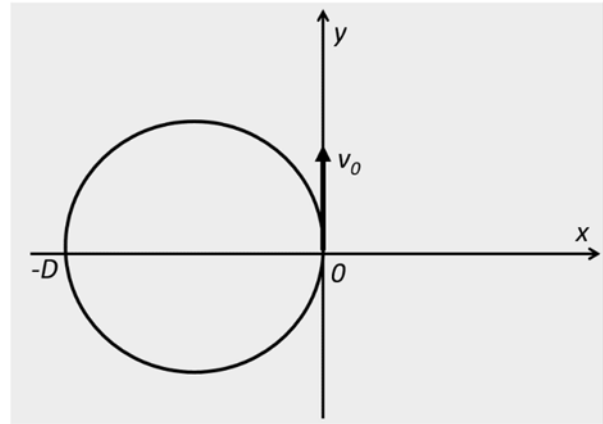

- (5) (b) Which of the following is the direction of the magnetic field? [Circle the correct answer.]

[A] \hat{i}
[E] $-\hat{i}$

[B] \hat{j}
[F] $-\hat{j}$

[C] \hat{k}
[G] $-\hat{k}$

[D] Clockwise
[H] Counterclockwise

- (10) (c) Calculate the magnitude of the magnetic flux through the area defined by the circular path.

$$\Phi_B = \int \vec{B} \cdot d\vec{A}$$

$$\Phi_B = \int B dA$$

$$\Phi_B = B \int dA$$

$$\Phi_B = BA$$

$$\Phi_B = \left(\frac{2m_e v_0}{eD} \right) \left[\pi \left(\frac{D}{2} \right)^2 \right]$$

$$\Phi_B = \frac{m_e v_0 \pi D}{2e}$$

- (10) (d) A positron (particle of mass m_e and charge $+e$) enters the same region with the same initial velocity $v = v_0$ along the positive y -axis. Find the position where the positron crosses the x -axis in its circular path.

$$x = +D$$