

Exam Total

/200

PHYS 2135 Exam II
October 15, 2019


Name: _____ Section: _____

For questions 1-5, select the best answer. For problems 6-9, solutions must begin with an Official Starting Equation, when appropriate. Work for problems must be shown and answers provided in the given boxes. Calculators are not allowed.

- (8) _____ 1. A 30 W light bulb and a 60 W are connected in series across a low-voltage power line. Which statement is true?
[A] The two bulbs draw the same current.
[B] The 30 W bulb draws a larger current than the 60 W bulb.
[C] The 60 W bulb draws a larger current than the 30 W bulb.
[D] This question cannot be answered without knowing the value of the voltage.
- (8) _____ 2. A fully charged parallel-plate capacitor is connected to a resistor R to form a resistor-capacitor (RC) circuit. Which of the following is true?
[A] The charge on the plates increases and the voltage across the capacitor increases.
[B] The charge on the plates decreases and the voltage across the capacitor decreases.
[C] The charge on the plates remains constant, but the voltage across the capacitor increases.
[D] The charge on the plates remains constant, but the voltage across the capacitor decreases.
- (8) _____ 3. To build a circuit you need a 1.5-Ohm resistor, but you only have at your disposal a box of 1-Ohm resistors. How do you combine three 1-Ohm resistors to make a 1.5-Ohm resistor?
[A] All three resistors in series.
[B] One resistor in parallel with two resistors connected in series.
[C] One resistor in series with two resistors connected in parallel.
[D] All three resistors in parallel.
- (8) _____ 4. A proton and an electron enter into a region of constant magnetic field \vec{B} with a velocity \vec{v} oriented perpendicular to \vec{B} . Which of the following statements describes the circular orbits of the two particles?
[A] The two orbits have the same radius and same direction.
[B] The two orbits have the same radius, but different direction.
[C] The two orbits have different radius, but same direction.
[D] The two orbits have different radius and different direction.
- (8) _____ 5 (Free). How many ears does Captain Kirk of the Star Trek Enterprise have:
[A] Two (his left ear and his right ear).
[B] One (only his left ear because a Gorn ate his right ear).
[C] One (only his right ear because a tribble nibbled his left ear).
[D] Three (his left ear, his right ear and his final front ear).

/40

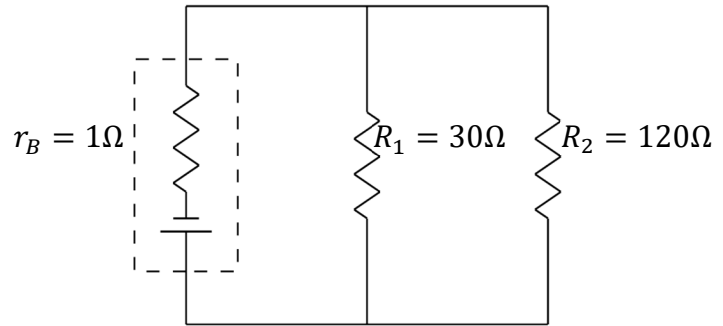6. A 10V battery with an internal resistance $r_B = 1.0\Omega$ is connected to two resistors $R_1 = 30\Omega$ and $R_2 = 120\Omega$ as illustrated.



- | | | (value) | (units) |
|------|---|--|---------|
| (10) | (a) Determine the total resistance of the circuit including the internal resistance of the battery. | <div style="border: 1px solid black; width: 100%; height: 40px; position: relative;"> <div style="position: absolute; top: 50%; left: 50%; transform: translate(-50%, -50%); border-left: 1px dashed black; border-right: 1px dashed black; width: 1px;"></div> </div> | |
| (10) | (b) Determine the total current through the circuit. | <div style="border: 1px solid black; width: 100%; height: 40px; position: relative;"> <div style="position: absolute; top: 50%; left: 50%; transform: translate(-50%, -50%); border-left: 1px dashed black; border-right: 1px dashed black; width: 1px;"></div> </div> | |
| (10) | (c) Determine the current through R_1 . | <div style="border: 1px solid black; width: 100%; height: 40px; position: relative;"> <div style="position: absolute; top: 50%; left: 50%; transform: translate(-50%, -50%); border-left: 1px dashed black; border-right: 1px dashed black; width: 1px;"></div> </div> | |
| (10) | (d) Determine the rate at which chemical energy is converted into electrical energy. | <div style="border: 1px solid black; width: 100%; height: 40px; position: relative;"> <div style="position: absolute; top: 50%; left: 50%; transform: translate(-50%, -50%); border-left: 1px dashed black; border-right: 1px dashed black; width: 1px;"></div> </div> | |

/40

7. A light bulb is connected across a 100V source. When it is first turned on at 20°C it dissipates a power of 100W. After several minutes, the light bulb filament reaches its operating temperature of 3000°C. The light bulb filament has a temperature coefficient of resistivity of $\alpha = 1/2980(\text{°C})^{-1}$. [You may neglect thermal expansion of the filament.]

(8) (a) Calculate the initial current passing through the 20°C filament.

(value)	(units)

(8) (b) Calculate the resistance of the 20°C filament

--	--

(8) (c) Calculate the resistance of the 3000°C filament

--	--

(8) (d) Calculate the power dissipated by the 3000°C bulb.


--	--

(8) (e) Calculate the current passing through the 3000°C filament.

--	--

/40




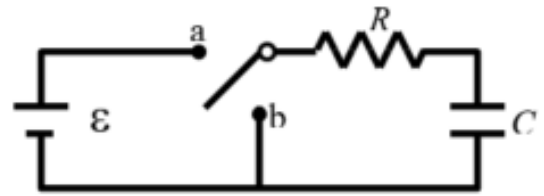
8. In the circuit shown with a resistance R , capacitance C , a switch S , and a battery with an emf \mathcal{E} , the capacitor is initially uncharged. Ignore the internal resistance of the battery.



- (8) (a) What is the initial current through the resistor immediately after the switch is set to position "a"?





- (8) (b) What will be the charge on the capacitor a long time after the switch is moved to position "a"?

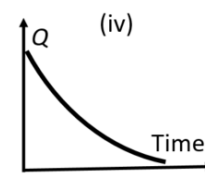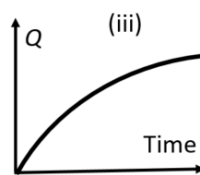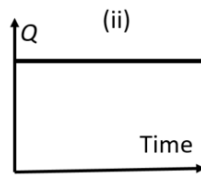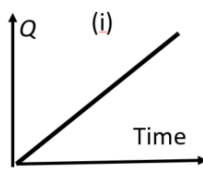- (8) (c) Which of the plots below best represents the charge on the capacitor as a function of time after the switch is moved to position "a"? (**circle one**)




- (8) (d) After the capacitor is fully charged, the switch is set to position "b". How much time is required for the charge on the capacitor to drop by a factor of $1/e$?

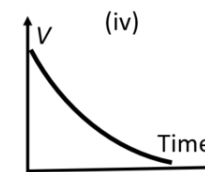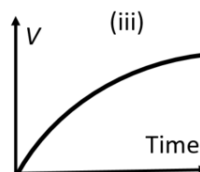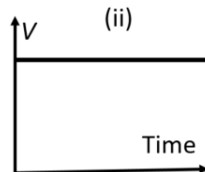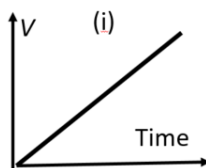- (8) (e) Which of the plots below best represents the voltage across the resistor as a function of time after the switch is set to position "b"? (**circle one**)



/40

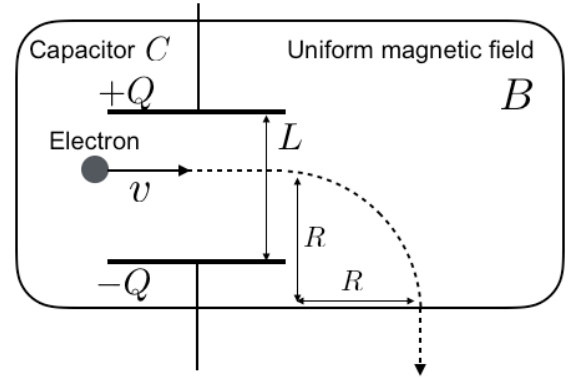9. A parallel plate capacitor with a distance L and a capacitance of C is charged with Q . The capacitor is placed in a uniform magnetic field B . An electron (charge $-e$, mass m) enters into the capacitor with a speed of v , and passes undeflected as shown. Express your answers using given symbols.



- (10) (a) Determine the magnitude and the direction of the electric field in the capacitor.

Direction. Circle one: (up) (down) (left) (right)

- (10) (b) Determine the magnitude and the direction of the magnetic force acting on the electron. Express your answer using B .

Direction. Circle one: (up) (down) (into the page) (out of the page)

- (10) (c) Determine the magnitude and the direction of the magnetic field. Express your answer using E .

Direction. Circle one: (up) (down) (into the page) (out of the page)

- (10) (d) After passing the capacitor, the electron experiences a quarter circular motion as shown. Determine the radius of the motion. Express your answer using B .