

<b>Exam Total</b>
<b>/200</b>

**PHYS 2135 Exam II**  
**October 15, 2019**


Name: \_\_\_\_\_ Section: \_\_\_\_\_

For questions 1-5, select the best answer. For problems 6-9, solutions must begin with an Official Starting Equation, when appropriate. Work for problems must be shown and answers provided in the given boxes. Calculators are not allowed.

- (8)   A   **1.** A 30 W light bulb and a 60 W are connected in series across a low-voltage power line. Which statement is true?  
[A] The two bulbs draw the same current.  
[B] The 30 W bulb draws a larger current than the 60 W bulb.  
[C] The 60 W bulb draws a larger current than the 30 W bulb.  
[D] This question cannot be answered without knowing the value of the voltage.
- (8)   B   **2.** A fully charged parallel-plate capacitor is connected to a resistor R to form a resistor-capacitor (RC) circuit. Which of the following is true?  
[A] The charge on the plates increases and the voltage across the capacitor increases.  
[B] The charge on the plates decreases and the voltage across the capacitor decreases.  
[C] The charge on the plates remains constant, but the voltage across the capacitor increases.  
[D] The charge on the plates remains constant, but the voltage across the capacitor decreases.
- (8)   C   **3.** To build a circuit you need a 1.5-Ohm resistor, but you only have at your disposal a box of 1-Ohm resistors. How do you combine three 1-Ohm resistors to make a 1.5-Ohm resistor?  
[A] All three resistors in series.  
[B] One resistor in parallel with two resistors connected in series.  
[C] One resistor in series with two resistors connected in parallel.  
[D] All three resistors in parallel.
- (8)   D   **4.** A proton and an electron enter into a region of constant magnetic field  $\vec{B}$  with a velocity  $\vec{v}$  oriented perpendicular to  $\vec{B}$ . Which of the following statements describes the circular orbits of the two particles?  
[A] The two orbits have the same radius and same direction.  
[B] The two orbits have the same radius, but different direction.  
[C] The two orbits have different radius, but same direction.  
[D] The two orbits have different radius and different direction.
- (8) \_\_\_\_\_ **5 (Free).** How many ears does Captain Kirk of the Star Trek Enterprise have:  
[A] Two (his left ear and his right ear).  
[B] One (only his left ear because a Gorn ate his right ear).  
[C] One (only his right ear because a tribble nibbled his left ear).  
[D] Three (his left ear, his right ear and his final front ear).

<b>/40</b>
------------

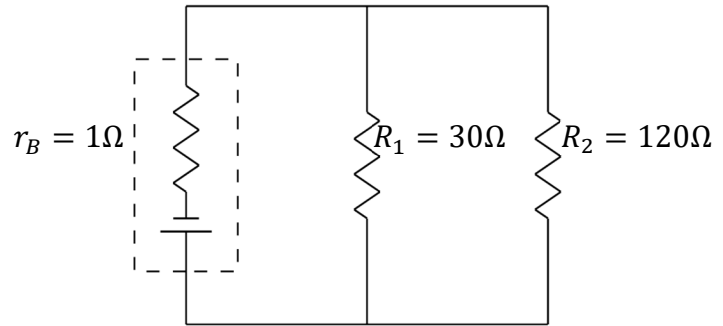6. A 10V battery with an internal resistance  $r_B = 1.0\Omega$  is connected to two resistors  $R_1 = 30\Omega$  and  $R_2 = 120\Omega$  as illustrated.



- (10) (a) Determine the total resistance of the circuit including the internal resistance of the battery.

$$R_{12} = \left( \frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} = \left( \frac{1}{30\Omega} + \frac{1}{120\Omega} \right)^{-1} = 24\Omega$$

$$R_T = R_{12} + r_B = 24\Omega + 1\Omega = 25\Omega$$

(value) (units)

$R_T = 25\Omega$
------------------

- (10) (b) Determine the total current through the circuit.

$$I_T = \frac{\mathcal{E}}{R_T} = \frac{10V}{25\Omega} = 0.4A$$

$I_T = 0.4A$
--------------

- (10) (c) Determine the current through  $R_1$ .

$$V_1 = \mathcal{E} - V_r = \mathcal{E} - I_T r_B = 10V - (.4A)(1\Omega) = 9.6V$$

$$I_1 = \frac{V_1}{R_1} = \frac{9.6V}{30\Omega} = 0.32A$$

$I_1 = 0.32A$
---------------

- (10) (d) Determine the rate at which chemical energy is converted into electrical energy.

$$P_{\mathcal{E}} = I_T \mathcal{E} = (.4A)(10V) = 4W$$

$P_{\mathcal{E}} = 4W$
------------------------

/40
-----

7. A light bulb is connected across a 100V source. When it is first turned on at 20°C it dissipates a power of 100W. After several minutes, the light bulb filament reaches its operating temperature of 3000°C. The light bulb filament has a temperature coefficient of resistivity of  $\alpha = 1/2980(\text{°C})^{-1}$ . [You may neglect thermal expansion of the filament.]

- (8) (a) Calculate the initial current passing through the 20°C filament.

(value)	(units)
$I_0 = 1.0$	A

OSE:  $P = IV$

$I_0 = P_0 / V = 100 \text{ W} / 100 \text{ V} = 1.0 \text{ A}$

Or OSE:  $V = IR, P = V^2 / R$

$R_0 = V^2 / P_0 = 100^2 / 100 = 100 \text{ ohm}$

$I_0 = V / R_0 = 100 \text{ V} / 100 \text{ ohm} = 1.0 \text{ A}$

- (8) (b) Calculate the resistance of the 20°C filament

$R_0 = 100\Omega$
-------------------

OSE:  $P = V^2 / R, R_0 = V^2 / P_0 = 100^2 / 100 = 100 \text{ ohm}$

- (8) (c) Calculate the resistance of the 3000°C filament

$R_f = 200\Omega$
-------------------

OSE:  $R_f = R_0(1 + \alpha(T_f - T_0))$

$R_f = R_0(1 + \alpha(T_f - T_0)) = 100(1 + (1/2980)(3000 - 20)) = 200 \text{ ohm}$

- (8) (d) Calculate the power dissipated by the 3000°C bulb.

$P_f = 50\text{W}$
--------------------

OSE:  $P = V^2 / R, P_f = V^2 / R_f = 100^2 / 200 = 50 \text{ W}$

Or:  $P = I^2R, I_f = V / R_f = 100 / 200 = 0.5 \text{ A}, P_f = (0.5^2)(200) = 200/4 = 50 \text{ W}$

Or:  $P = P_0 / (1 + \alpha(T_f - T_0)) = 100 / (1 + (1/2980)(3000 - 20)) = 50 \text{ W}$

- (8) (e) Calculate the current passing through the 3000°C filament.


$I_f = 0.5\text{A}$
---------------------

OSE:  $P = IV, I_f = P_f / V = 50 / 100 = 0.5 \text{ A}$

or OSE:  $V = IR, I_f = V / R_f = 100 / 200 = 0.5 \text{ A}$

<b>/40</b>
------------

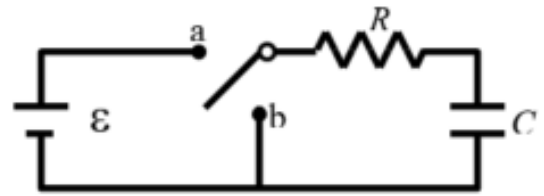8. In the circuit shown with a resistance  $R$ , capacitance  $C$ , a switch  $S$ , and a battery with an emf  $\mathcal{E}$ , the capacitor is initially uncharged. Ignore the internal resistance of the battery.



- (8) (a) What is the initial current through the resistor immediately after the switch is set to position “a”?

$$I_0 = \frac{\mathcal{E}}{R}$$

$$\mathcal{E} - I_0 R + 0 = 0$$

$$I_0 = \frac{\mathcal{E}}{R}$$

- (8) (b) What will be the charge on the capacitor a long time after the switch is moved to position “a”?


$$Q_f = C\mathcal{E}$$

$$\mathcal{E} - IR + V_C = 0$$

$$|V_C| = \mathcal{E}$$

$$Q_f = CV = C\mathcal{E}$$

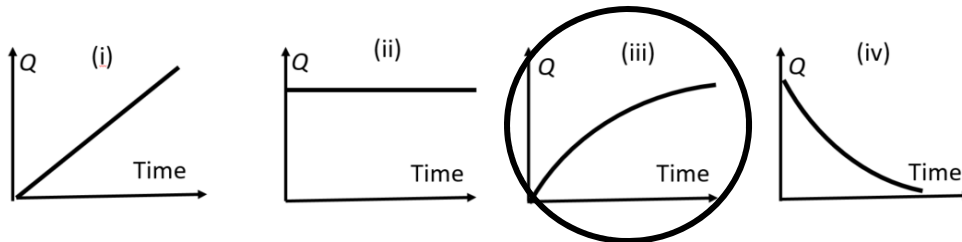- (8) (c) Which of the plots below best represents the charge on the capacitor as a function of time after the switch is moved to position “a”? **(circle one)**




- (8) (d) After the capacitor is fully charged, the switch is set to position “b”. How much time is required for the charge on the capacitor to drop by a factor of  $1/e$ ?


$$t = RC$$

$$\frac{Q}{Q_0} = e^{-t/RC} = \frac{1}{e} \quad \frac{t}{RC} = 1 \quad t = RC \quad Q = Q_0 e^{-t/RC}$$

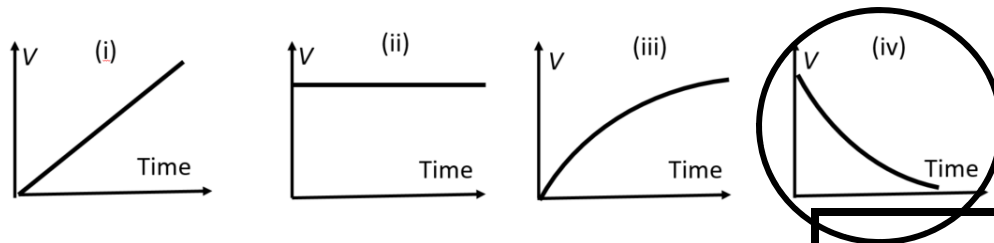- (8) (e) Which of the plots below best represents the voltage across the resistor as a function of time after the switch is set to position “b”? **(circle one)**



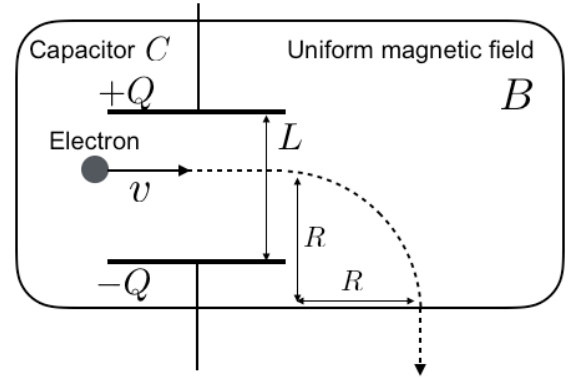9. A parallel plate capacitor with a distance  $L$  and a capacitance of  $C$  is charged with  $Q$ . The capacitor is placed in a uniform magnetic field  $B$ . An electron (charge  $-e$ , mass  $m$ ) enters into the capacitor with a speed of  $v$ , and passes undeflected as shown. Express your answers using given symbols.



- (10) (a) Determine the magnitude and the direction of the electric field in the capacitor.

$$V = \frac{Q}{C}$$

$$\Delta V = - \int \vec{E} \cdot d\vec{s} \quad V = |EL|$$

$$E = \frac{Q}{CL}$$

$$E = \frac{V}{L} = \frac{Q}{CL}$$

Direction. Circle one: (up) (down) (left) (right)

- (10) (b) Determine the magnitude and the direction of the magnetic force acting on the electron. Express your answer using  $B$ .

$$F_B = evB$$

$$\vec{F}_B = q\vec{v} \times \vec{B}$$

Direction. Circle one: (up) (down) (into the page) (out of the page)

- (10) (c) Determine the magnitude and the direction of the magnetic field. Express your answer using  $E$ .

$$B = \frac{E}{v}$$

$$\vec{F}_B = -\vec{F}_E = -q\vec{E}$$

$$eE = evB$$

$$B = \frac{E}{v}$$

Direction. Circle one: (up) (down) (into the page) (out of the page)

- (10) (d) After passing the capacitor, the electron experiences a quarter circular motion as shown. Determine the radius of the motion. Express your answer using  $B$ .

$$r = \frac{mv}{eB}$$

$$\frac{mv^2}{r} = F_r = evB$$

$$r = \frac{mv}{eB}$$