
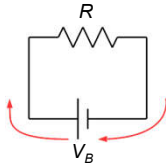


Simple Circuits

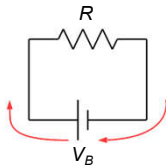


Simple Circuits




Charges leaving the battery have more energy than charges entering battery. Consider $V = \frac{U}{q}$
 $V_{\text{Leaving}} = V_{\text{Entering}} + V_B$

Simple Circuits

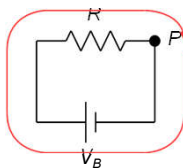

The sum of voltage changes around a loop is 0.
 $\Delta V = V_P - V_P = 0$

Simple Circuits

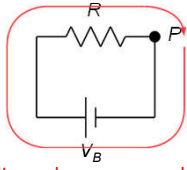


The sum of voltage changes around a loop is 0.

$$\Delta V = V_P - V_P = 0$$

Kirchhoff's Loop Rule, $\sum_i \Delta V_i = 0$

Simple Circuits

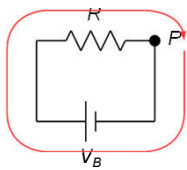


$V_B + V_R = 0$
 V_R is negative.

From previous lecture, $|V_R| = IR$.

$V_R = -IR$

Simple Circuits

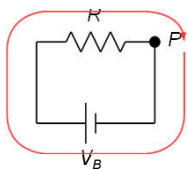


$V_B + V_R = 0$
 V_R is negative.

From previous lecture, $|V_R| = IR$.

$V_R = -IR$

We often write $V = IR$ when we mean $|\Delta V| = |IR|$, but one must be precise when adding around a loop in a circuit.

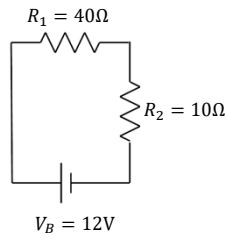Example: Determine the current in the given circuit.





Strategy


Select and label a direction for current.

Select a direction for summation.


Add ΔV 's.

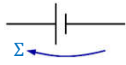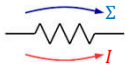- V_B is positive going from - to + 
- V_R is negative going with current 

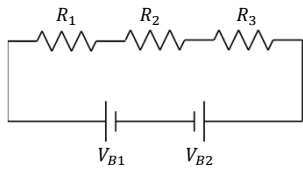Example: Determine the current in the given circuit.



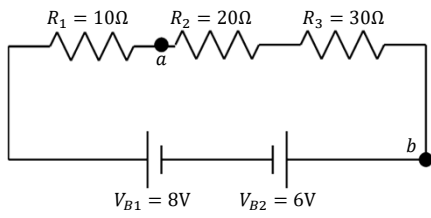Example: For the given circuit, determine I , V_{ab} and V_{ba} .



$$V_{ab} = \Delta V_{ab} = V_b - V_a$$
