
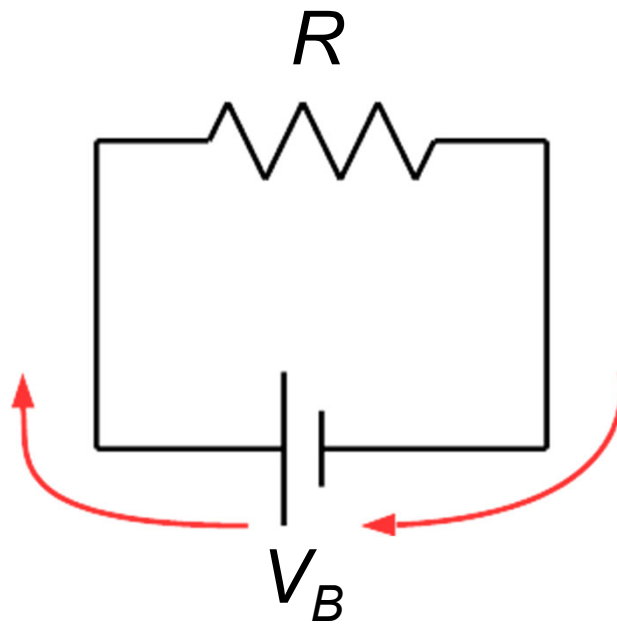


# Simple Circuits

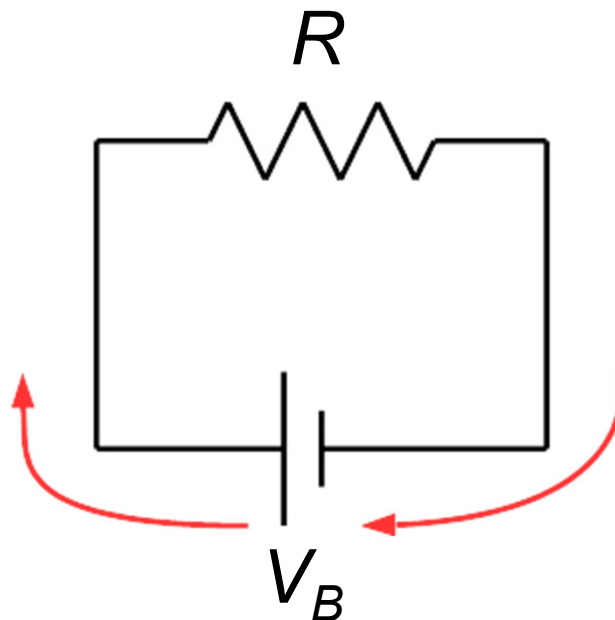


## Simple Circuits



Charges leaving the battery have more energy than charges entering battery. Consider  $V = \frac{U}{q}$

$$V_{\text{Leaving}} = V_{\text{Entering}} + V_B$$


## Simple Circuits

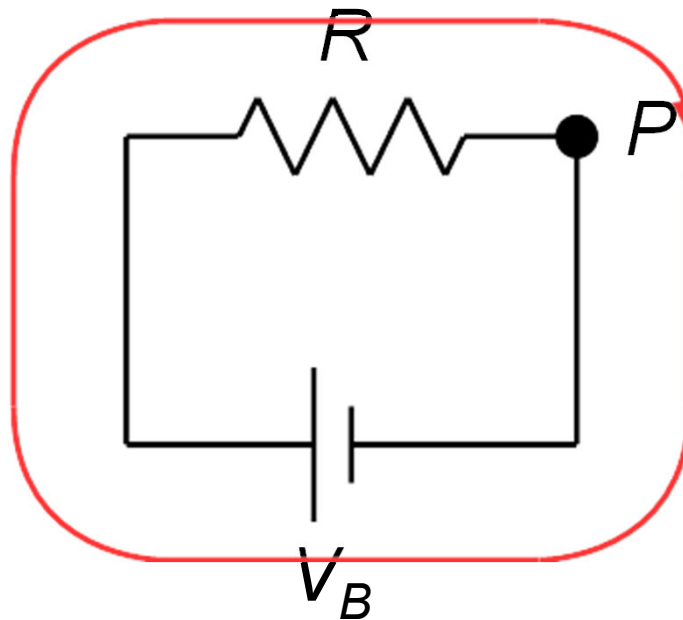

The sum of voltage changes around a loop is 0.

$$\Delta V = V_P - V_P = 0$$

## Simple Circuits

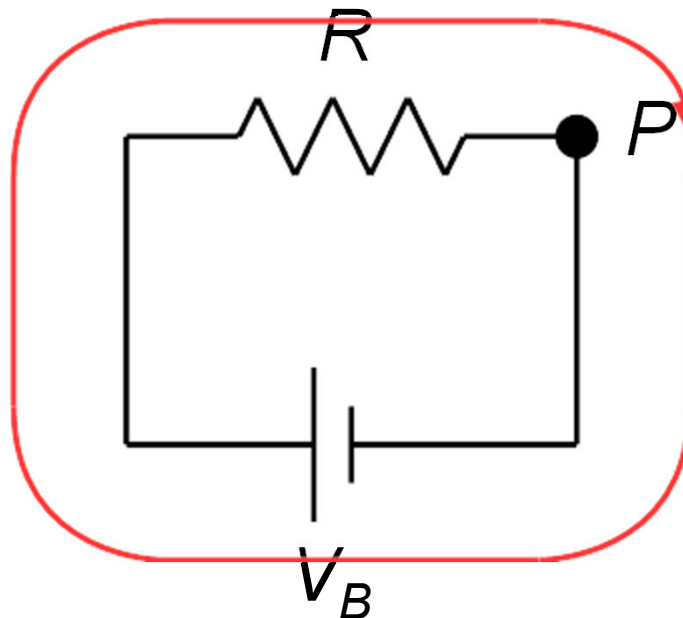


The sum of voltage changes around a loop is 0.

$$\Delta V = V_P - V_P = 0$$

Kirchhoff's Loop Rule,  $\sum_i \Delta V_i = 0$

## Simple Circuits

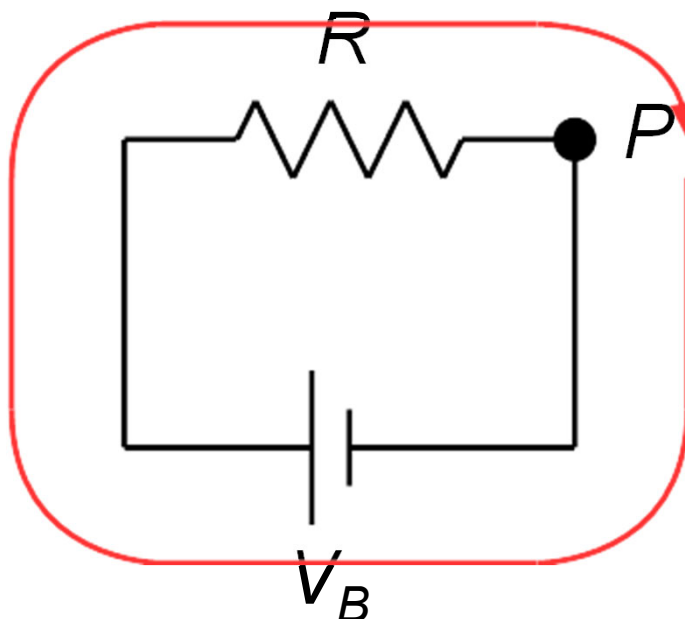


$$V_B + V_R = 0$$

$V_R$  is negative.

From previous lecture,  $|V_R| = IR$ .

$$V_R = -IR$$

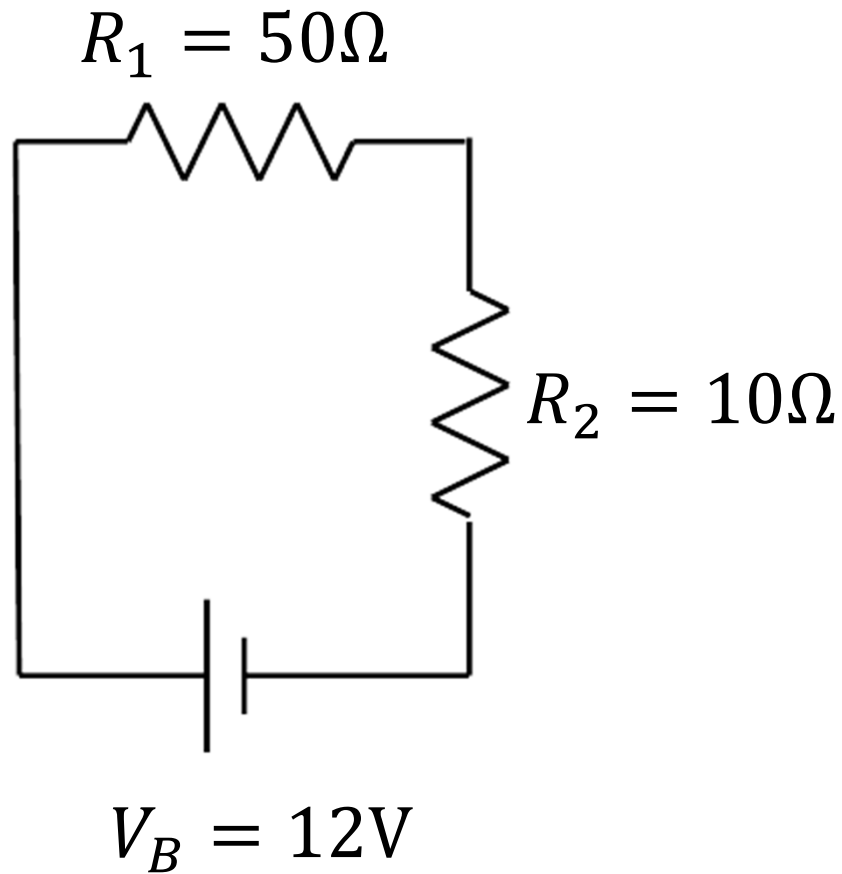Example: Determine the current in the given circuit.




## Strategy

Select and label a direction for current.


Select a direction for summation.

Add  $\Delta V$ 's.

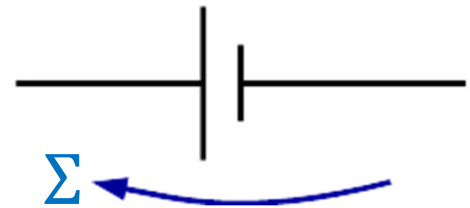
- $V_B$  is positive going from  $-$  to  $+$



- $V_R$  is negative going with current

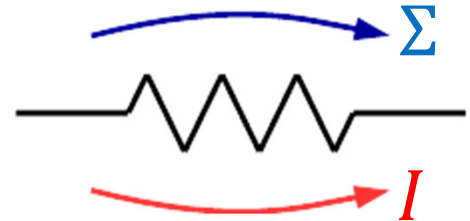


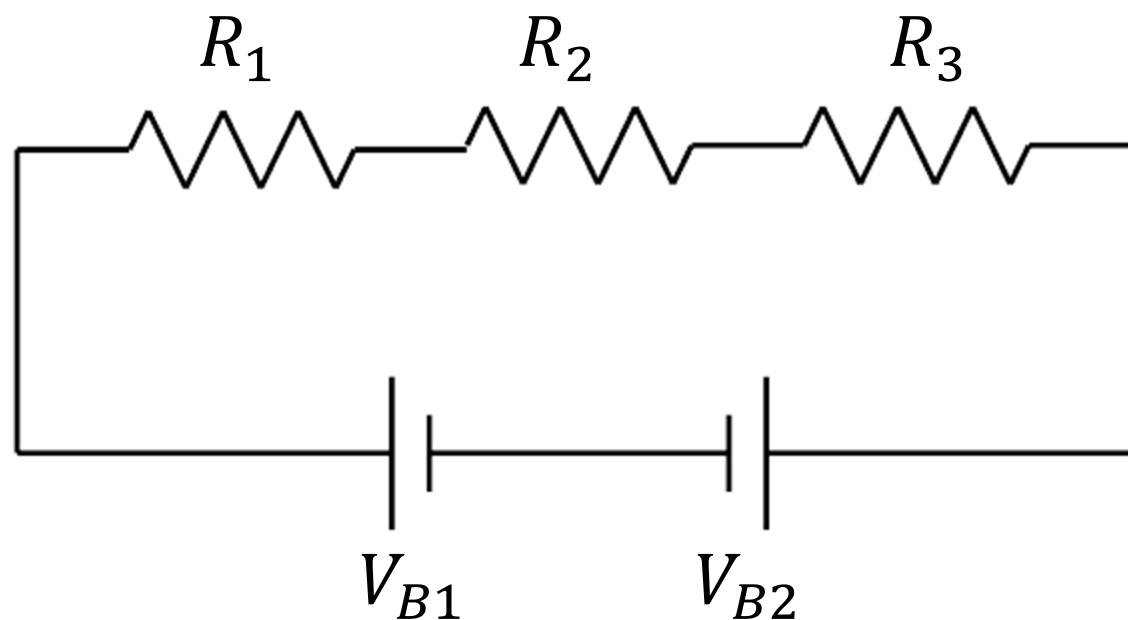Example: Determine the current in the given circuit.





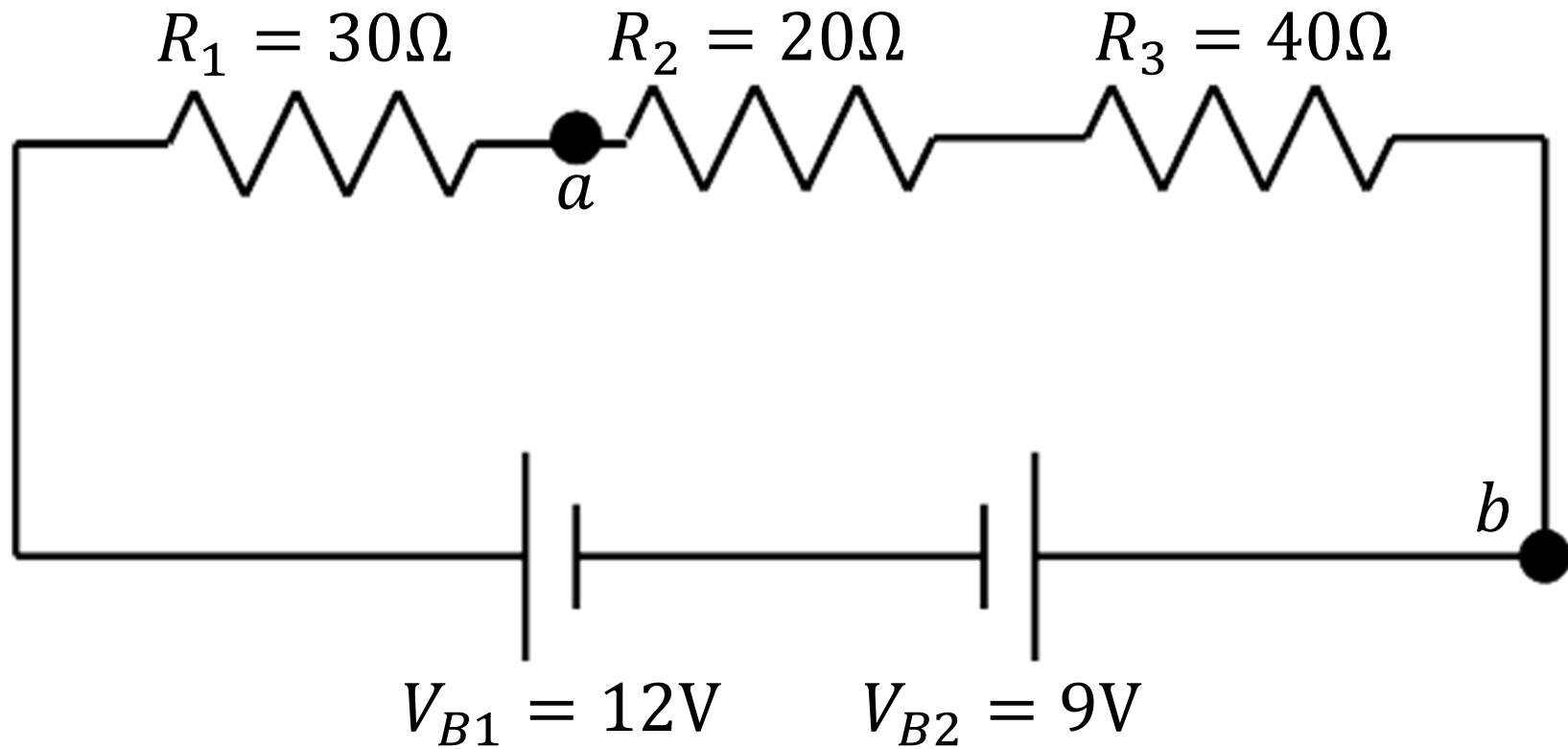Example: For the given circuit, determine  $I$ ,  $V_{ab}$  and  $V_{ba}$ .



$$V_{ab} = \Delta V_{ab} = V_b - V_a$$


## Real Batteries

- Have internal resistance
- Voltage depends on current

## Real Batteries

- Have internal resistance
- Voltage depends on current

Model of a real battery:

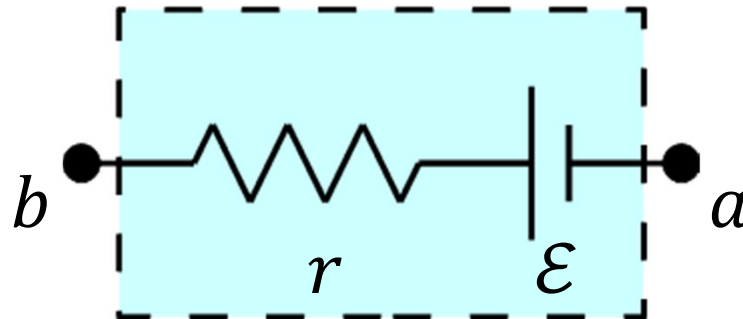


$\mathcal{E}$  is the ideal  $V$  of the battery.

$r$  is the internal resistance of the battery.

$V_{ab}$  is the real  $V$  of the battery.
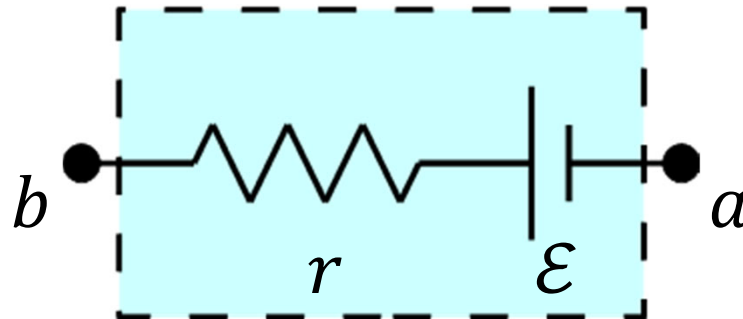
## Electromotive Force, $\mathcal{E}$ (emf)


- Is not a force
- Cannot be directly measured



Can only measure terminal voltage,  $V_{ab}$ .

$V_{ab}$  is a function of current.  $V_{ab} = \mathcal{E} - Ir$

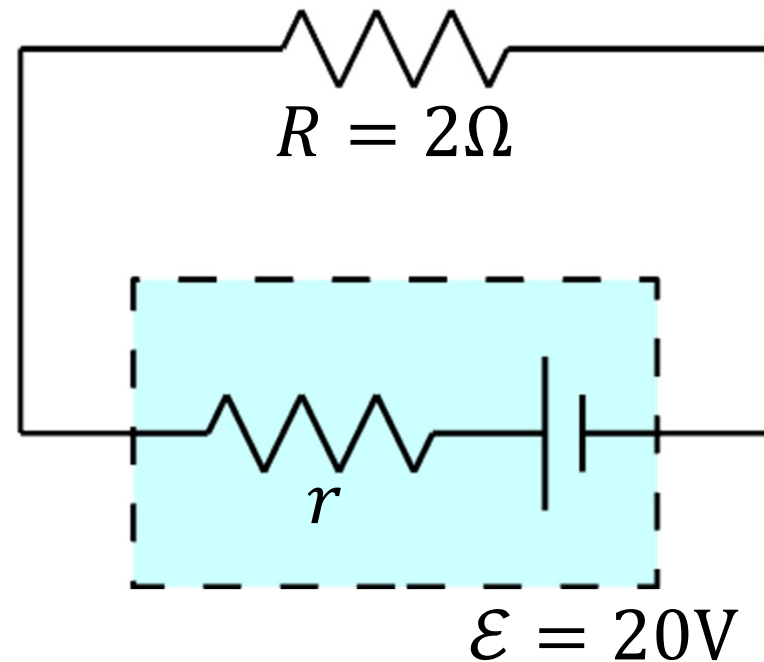Example: The terminal voltage of a “20V” battery is found to be 16V when connected in a circuit with a  $2\Omega$  resistor. Determine the internal resistance of the battery.



# Power

$$P = \frac{dW}{dt}$$

$$W = \Delta U = q\Delta V$$

$$P = \frac{dq\Delta V}{dt}$$

$$P = I\Delta V$$

$$P = IV = I^2R = \frac{V^2}{R}$$

## Power

$$P = IV = I^2R = \frac{V^2}{R}$$

Rate of energy production in battery. ( $V_B > 0$ )

Rate of energy dissipation in resistor. ( $V_R < 0$ )

Example: An electric heater draws 15A on a 120V line.  
(a) How much power does the heater use?



Example: An electric heater draws 15A on a 120V line.  
(a) How much power does the heater use? (b) The cost of electricity is 10.5 cents per kWh. How much does it cost to run the heater 3 hours a day for a 30-day month?

Example: An electric heater draws 15A on a 120V line.  
(a) How much power does the heater use? (b) The cost of electricity is 10.5 cents per kWh. How much does it cost to run the heater 3 hours a day for a 30-day month?


How much energy is a kilowatt hour?

Example: A 12V battery with  $2\Omega$  internal resistance is connected to a  $4\Omega$  resistor. (a) Determine the rate at which chemical energy is converted to electrical energy in the battery. (b) Determine the rate at which power is dissipated internally in the battery. (c) Determine the total power output of the battery.

## Power Ratings
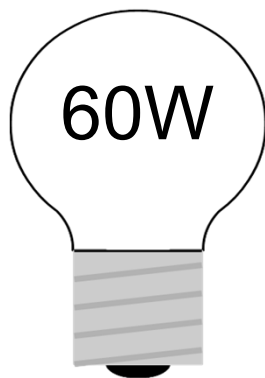
### Light bulbs are rated by power

- Rated power and dissipated power may differ
- Rated power is for specific voltage
- Dissipated power depends on voltage
- Usually better to describe bulbs by resistance



$$P = 60\text{W} \text{ IF } V = 120\text{V} \quad (I = 0.5\text{A})$$


$$R = 240\Omega$$

$$P = 202\text{W} \text{ IF } V = 220\text{V} \quad (I = 0.9\text{A})$$


## Power Ratings

Light bulbs are rated by power

- Higher power rating → lower resistance

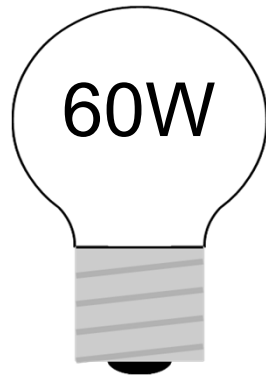
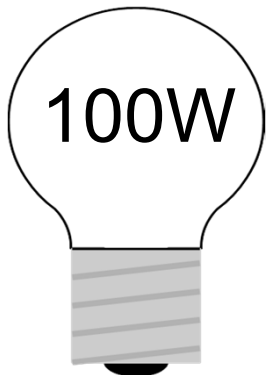
$$P = 60\text{W} \text{ IF } V = 120\text{V} \quad (I = 0.5\text{A})$$
$$R = 240\Omega$$



$$P = 100\text{W} \text{ IF } V = 120\text{V} \quad (I = 0.8\text{A})$$
$$R = 144\Omega$$