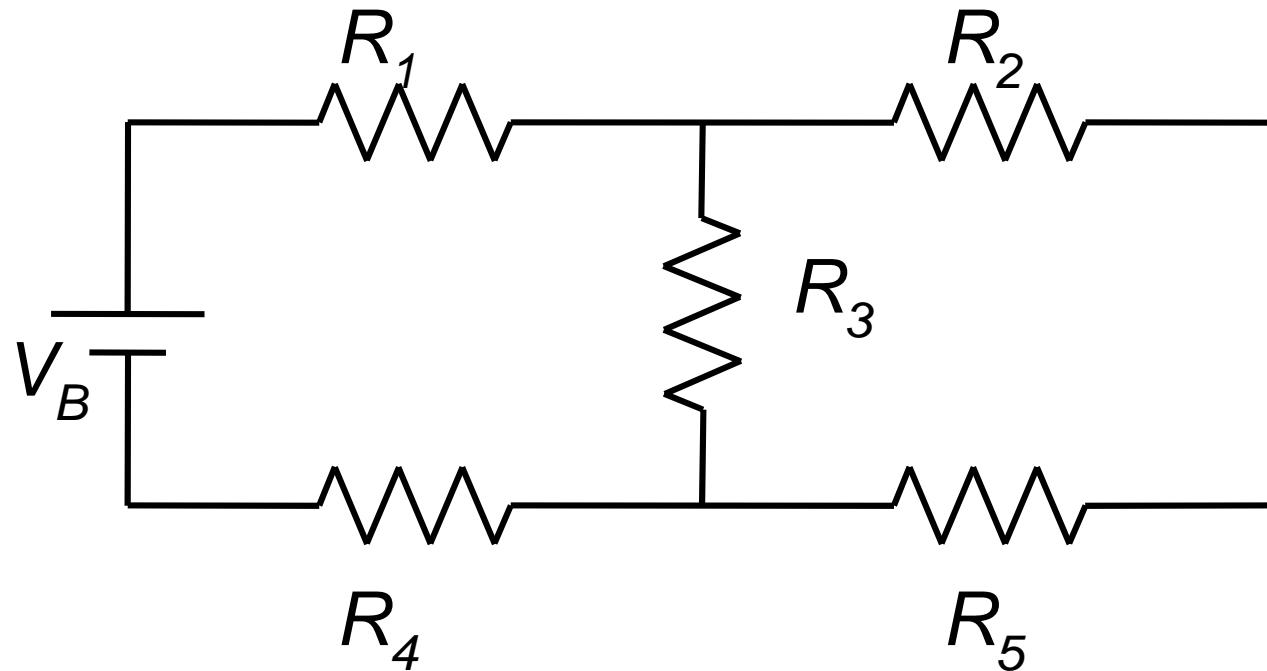


Determine the current through each resistor, the total current and the voltage across each resistor.



$$V_B = 24 \text{ V}$$

$$R_1 = 84 \Omega$$


$$R_2 = 51 \Omega$$

$$R_3 = 96 \Omega$$

$$R_4 = 35 \Omega$$

$$R_5 = 75 \Omega$$

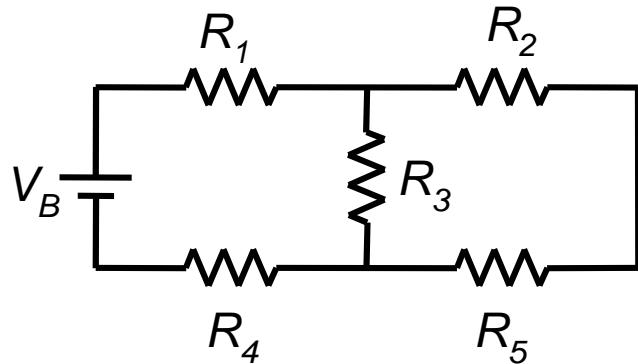Determine the current through each resistor, the total current and the voltage across each resistor.



Determine equivalent resistance.

Note:

- Every charge goes through R_1 .
- Charges go through either R_3 or R_2 and R_5 .
- Every charge goes through R_4 .

$$V_B = 24 \text{ V}$$

$$R_1 = 84 \Omega$$


$$R_2 = 51 \Omega$$

$$R_3 = 96 \Omega$$

$$R_4 = 35 \Omega$$

$$R_5 = 75 \Omega$$

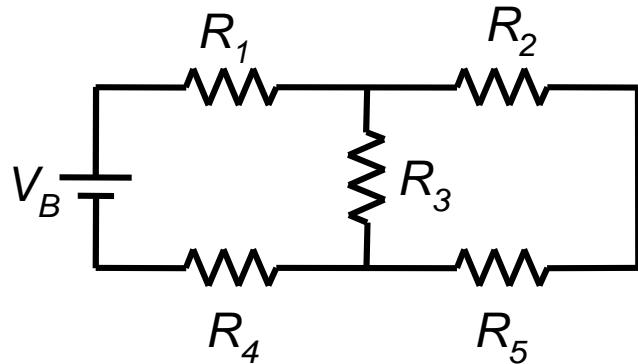Determine the current through each resistor, the total current and the voltage across each resistor.



Determine equivalent resistance.

Note:

- Every charge goes through R_1 .
- Charges go through either R_3 or R_2 and R_5 .
- Every charge goes through R_4 .

$$V_B = 24 \text{ V}$$

$$R_1 = 84 \Omega$$

$$R_2 = 51 \Omega$$

$$R_3 = 96 \Omega$$

$$R_4 = 35 \Omega$$


$$R_5 = 75 \Omega$$

R_2 is in series with R_5 .

R_3 is in parallel with R_{25} .

R_1 is in series with R_{325} and R_4 .

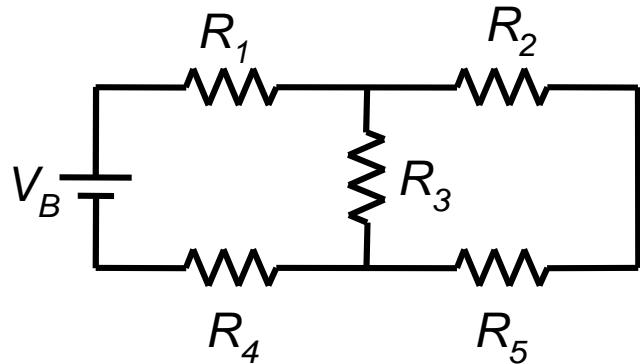Determine the current through each resistor, the total current and the voltage across each resistor.



$$R_{25} = R_2 + R_5$$

$$R_{25} = 51\Omega + 75\Omega$$

$$R_{25} = 126\Omega$$

$$V_B = 24\text{ V} \quad R_{25} = 126\Omega$$

$$R_1 = 84\Omega$$


$$R_2 = 51\Omega$$

$$R_3 = 96\Omega$$

$$R_4 = 35\Omega$$

$$R_5 = 75\Omega$$

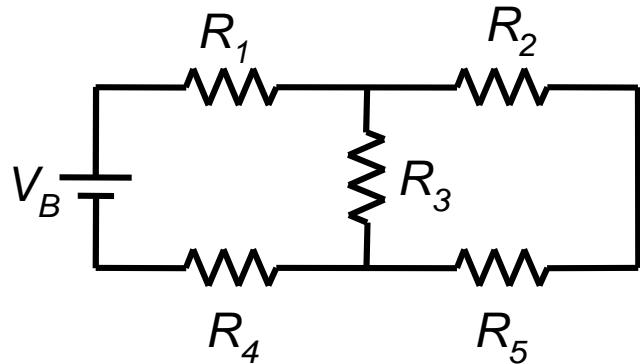Determine the current through each resistor, the total current and the voltage across each resistor.



$$R_{325} = (R_3^{-1} + R_{25}^{-1})^{-1}$$

$$R_{325} = [(96\Omega)^{-1} + (126\Omega)^{-1}]$$

$$R_{325} = 54\Omega$$

$$V_B = 24\text{ V} \quad R_{25} = 126\Omega$$

$$R_1 = 84\Omega \quad R_{325} = 54\Omega$$


$$R_2 = 51\Omega$$

$$R_3 = 96\Omega$$

$$R_4 = 35\Omega$$

$$R_5 = 75\Omega$$

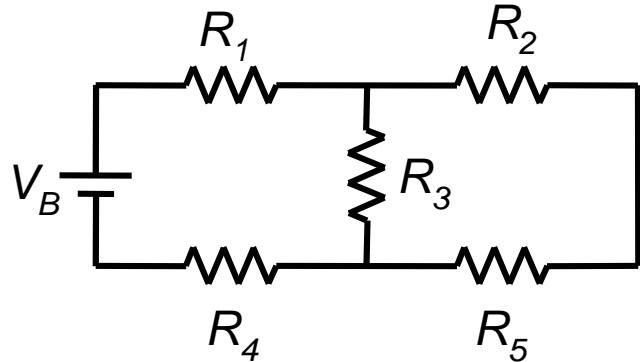Determine the current through each resistor, the total current and the voltage across each resistor.



$$R_T = R_1 + R_{325} + R_4$$

$$R_T = 84\Omega + 54\Omega + 35\Omega$$

$$R_T = 173\Omega$$

$$V_B = 24\text{ V} \quad R_{25} = 126\Omega$$

$$R_1 = 84\Omega \quad R_{325} = 54\Omega$$


$$R_2 = 51\Omega \quad R_T = 173\Omega$$

$$R_3 = 96\Omega$$

$$R_4 = 35\Omega$$

$$R_5 = 75\Omega$$

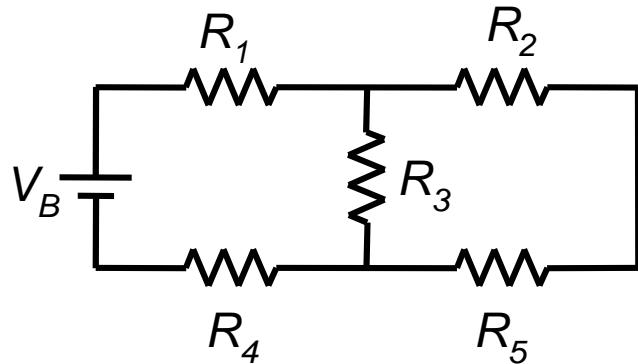Determine the current through each resistor, the total current and the voltage across each resistor.



Determine potential differences and currents.

$$V_B = 24 \text{ V} \quad R_{25} = 126 \Omega$$

$$R_1 = 84 \Omega \quad R_{325} = 54 \Omega$$


$$R_2 = 51 \Omega \quad R_T = 173 \Omega$$

$$R_3 = 96 \Omega$$

$$R_4 = 35 \Omega$$

$$R_5 = 75 \Omega$$

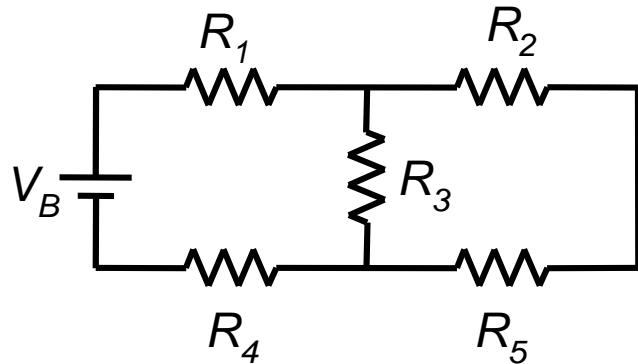Determine the current through each resistor, the total current and the voltage across each resistor.



$$I_T = \frac{V_B}{R_T}$$

$$I_T = \frac{24 \text{ V}}{173 \Omega}$$

$$V_B = 24 \text{ V} \quad R_{25} = 126 \Omega$$

$$R_1 = 84 \Omega \quad R_{325} = 54 \Omega$$

$$R_2 = 51 \Omega \quad R_T = 173 \Omega \quad I_T = 0.14 \text{ A}$$


$$R_3 = 96 \Omega$$

$$R_4 = 35 \Omega$$

$$R_5 = 75 \Omega$$

$$I_T = 0.14 \text{ A}$$

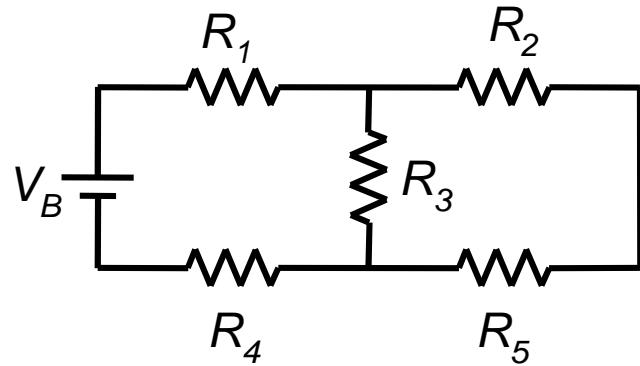Determine the current through each resistor, the total current and the voltage across each resistor.



Note that $I_T = I_1 = I_4$.

$$V_B = 24 \text{ V} \quad R_{25} = 126 \Omega$$

$$R_1 = 84 \Omega \quad R_{325} = 54 \Omega$$


$$R_2 = 51 \Omega \quad R_T = 173 \Omega \quad I_T = I_1 = I_4 = 0.14 \text{ A}$$

$$R_3 = 96 \Omega$$

$$R_4 = 35 \Omega$$

$$R_5 = 75 \Omega$$

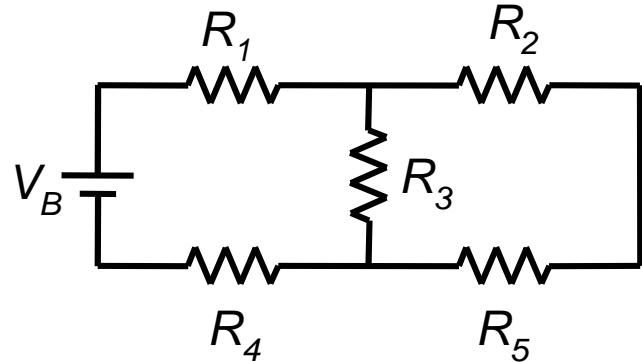Determine the current through each resistor, the total current and the voltage across each resistor.



$$V_1 = I_1 R_1$$

$$V_1 = (0.14 \text{ A})(84 \Omega)$$

$$V_1 = 12 \text{ V}$$

$$V_B = 24 \text{ V} \quad R_{25} = 126 \Omega$$

$$R_1 = 84 \Omega \quad R_{325} = 54 \Omega$$

$$R_2 = 51 \Omega \quad R_T = 173 \Omega \quad I_T = I_1 = I_4 = 0.14 \text{ A}$$


$$R_3 = 96 \Omega$$

$$R_4 = 35 \Omega$$

$$R_5 = 75 \Omega$$

$$V_1 = 12 \text{ V}$$

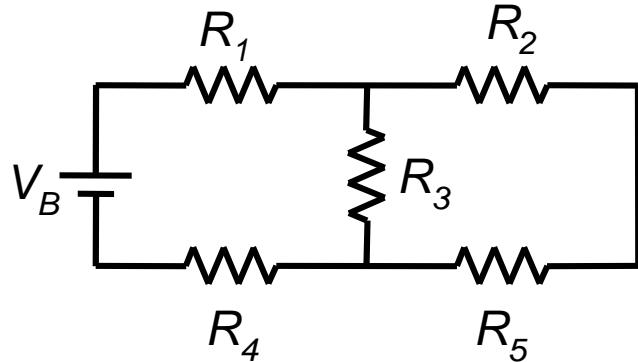Determine the current through each resistor, the total current and the voltage across each resistor.



$$V_4 = I_4 R_4$$

$$V_4 = (0.14 \text{ A})(35 \Omega)$$

$$V_4 = 5 \text{ V}$$

$$V_B = 24 \text{ V} \quad R_{25} = 126 \Omega$$

$$R_1 = 84 \Omega \quad R_{325} = 54 \Omega$$

$$R_2 = 51 \Omega \quad R_T = 173 \Omega \quad I_T = I_1 = I_4 = 0.14 \text{ A} \quad V_1 = 12 \text{ V}$$


$$R_3 = 96 \Omega$$

$$R_4 = 35 \Omega$$

$$R_5 = 75 \Omega$$

$$V_4 = 5 \text{ V}$$

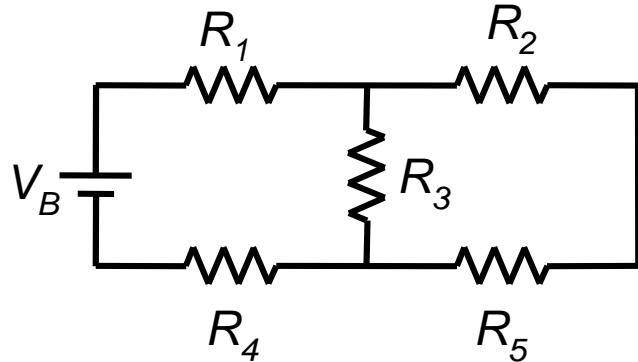Determine the current through each resistor, the total current and the voltage across each resistor.



$$V_{325} = V_B - V_1 - V_4$$

$$V_{325} = 24 \text{ V} - 12 \text{ V} - 5 \text{ V}$$

$$V_{325} = 7 \text{ V}$$

$$V_B = 24 \text{ V} \quad R_{25} = 126 \Omega$$

$$R_1 = 84 \Omega \quad R_{325} = 54 \Omega$$

$$R_2 = 51 \Omega \quad R_T = 173 \Omega$$

$$R_3 = 96 \Omega$$

$$R_4 = 35 \Omega$$


$$R_5 = 75 \Omega$$

$$V_1 = 12 \text{ V}$$

$$V_4 = 5 \text{ V}$$

$$V_{325} = 7 \text{ V}$$

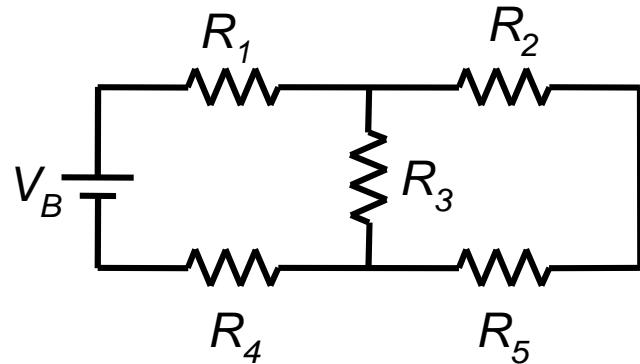Determine the current through each resistor, the total current and the voltage across each resistor.



Note that $V_{325} = V_3 = V_{25}$.

$$V_B = 24 \text{ V} \quad R_{25} = 126 \Omega$$

$$R_1 = 84 \Omega \quad R_{325} = 54 \Omega$$

$$R_2 = 51 \Omega \quad R_T = 173 \Omega \quad I_T = I_1 = I_4 = 0.14 \text{ A}$$

$$R_3 = 96 \Omega$$

$$R_4 = 35 \Omega$$


$$R_5 = 75 \Omega$$

$$V_1 = 12 \text{ V}$$

$$V_4 = 5 \text{ V}$$

$$V_{325} = V_3 = V_{25} = 7 \text{ V}$$

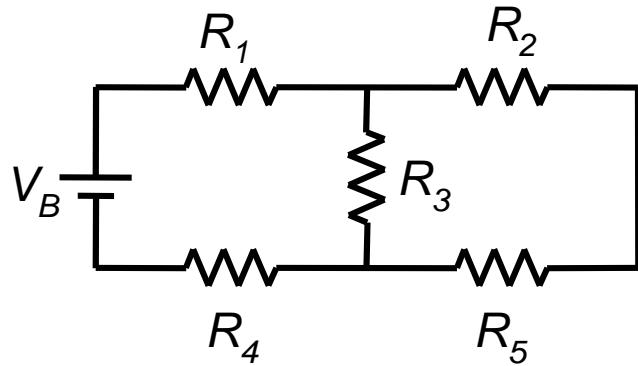Determine the current through each resistor, the total current and the voltage across each resistor.



$$I_3 = \frac{V_3}{R_3}$$

$$I_3 = \frac{7 \text{ V}}{96 \Omega}$$

$$I_3 = 0.07 \text{ A}$$

$$V_B = 24 \text{ V} \quad R_{25} = 126 \Omega$$

$$R_1 = 84 \Omega \quad R_{325} = 54 \Omega$$

$$R_2 = 51 \Omega \quad R_T = 173 \Omega$$

$$R_3 = 96 \Omega$$

$$R_4 = 35 \Omega$$

$$R_5 = 75 \Omega$$

$$I_T = I_1 = I_4 = 0.14 \text{ A}$$


$$I_3 = 0.07 \text{ A}$$

$$V_1 = 12 \text{ V}$$

$$V_4 = 5 \text{ V}$$

$$V_{325} = V_3 = V_{25} = 7 \text{ V}$$

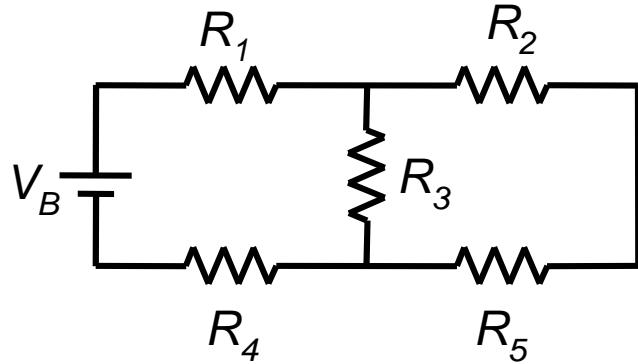Determine the current through each resistor, the total current and the voltage across each resistor.



$$I_{25} = \frac{V_{25}}{R_{25}}$$

$$I_{25} = \frac{7 \text{ V}}{126 \Omega}$$

$$I_{25} = 0.06 \text{ A}$$

$$V_B = 24 \text{ V} \quad R_{25} = 126 \Omega$$

$$R_1 = 84 \Omega \quad R_{325} = 54 \Omega$$

$$R_2 = 51 \Omega \quad R_T = 173 \Omega$$

$$R_3 = 96 \Omega$$

$$R_4 = 35 \Omega$$

$$R_5 = 75 \Omega$$

$$I_T = I_1 = I_4 = 0.14 \text{ A}$$

$$I_3 = 0.07 \text{ A}$$


$$I_{25} = 0.06 \text{ A}$$

$$V_1 = 12 \text{ V}$$

$$V_4 = 5 \text{ V}$$

$$V_{325} = V_3 = V_{25} = 7 \text{ V}$$

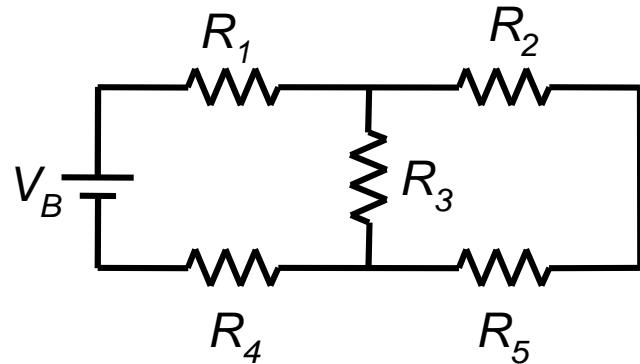Determine the current through each resistor, the total current and the voltage across each resistor.



Note that $I_{25} = I_2 = I_5$.

$$V_B = 24 \text{ V} \quad R_{25} = 126 \Omega$$

$$R_1 = 84 \Omega \quad R_{325} = 54 \Omega$$

$$R_2 = 51 \Omega \quad R_T = 173 \Omega$$

$$R_3 = 96 \Omega$$

$$R_4 = 35 \Omega$$

$$R_5 = 75 \Omega$$

$$I_T = I_1 = I_4 = 0.14 \text{ A}$$

$$I_3 = 0.07 \text{ A}$$


$$I_{25} = I_2 = I_5 = 0.06 \text{ A}$$

$$V_1 = 12 \text{ V}$$

$$V_4 = 5 \text{ V}$$

$$V_{325} = V_3 = V_{25} = 7 \text{ V}$$

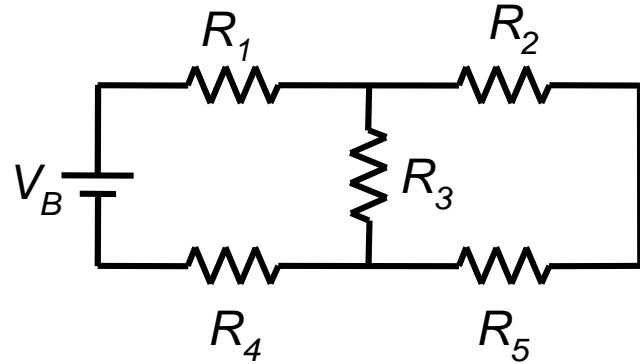Determine the current through each resistor, the total current and the voltage across each resistor.



$$V_2 = I_2 R_2$$

$$V_2 = (0.06 \text{ A})(51 \Omega)$$

$$V_2 = 3 \text{ V}$$

$$V_B = 24 \text{ V} \quad R_{25} = 126 \Omega$$

$$R_1 = 84 \Omega \quad R_{325} = 54 \Omega$$

$$R_2 = 51 \Omega \quad R_T = 173 \Omega$$

$$R_3 = 96 \Omega$$

$$R_4 = 35 \Omega$$

$$R_5 = 75 \Omega$$

$$I_T = I_1 = I_4 = 0.14 \text{ A}$$

$$I_3 = 0.07 \text{ A}$$

$$I_{25} = I_2 = I_5 = 0.06 \text{ A}$$


$$V_1 = 12 \text{ V}$$

$$V_4 = 5 \text{ V}$$

$$V_{325} = V_3 = V_{25} = 7 \text{ V}$$

$$V_2 = 3 \text{ V}$$

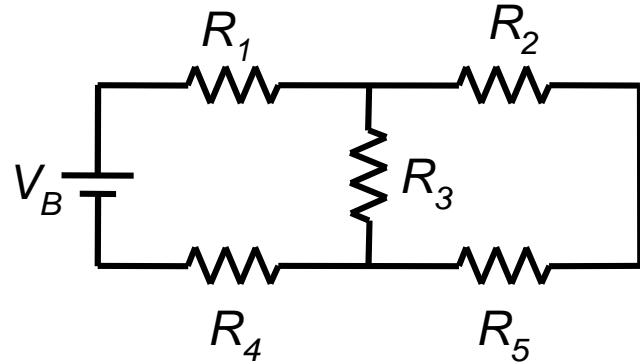Determine the current through each resistor, the total current and the voltage across each resistor.



$$V_5 = I_5 R_5$$

$$V_5 = (0.06 \text{ A})(75 \Omega)$$

$$V_5 = 5 \text{ V}$$

$$V_B = 24 \text{ V} \quad R_{25} = 126 \Omega$$

$$R_1 = 84 \Omega \quad R_{325} = 54 \Omega$$

$$R_2 = 51 \Omega \quad R_T = 173 \Omega$$

$$R_3 = 96 \Omega$$

$$R_4 = 35 \Omega$$

$$R_5 = 75 \Omega$$

$$I_T = I_1 = I_4 = 0.14 \text{ A}$$

$$I_3 = 0.07 \text{ A}$$

$$I_{25} = I_2 = I_5 = 0.06 \text{ A}$$

$$V_1 = 12 \text{ V}$$


$$V_4 = 5 \text{ V}$$

$$V_{325} = V_3 = V_{25} = 7 \text{ V}$$

$$V_2 = 3 \text{ V}$$

$$V_5 = 5 \text{ V}$$

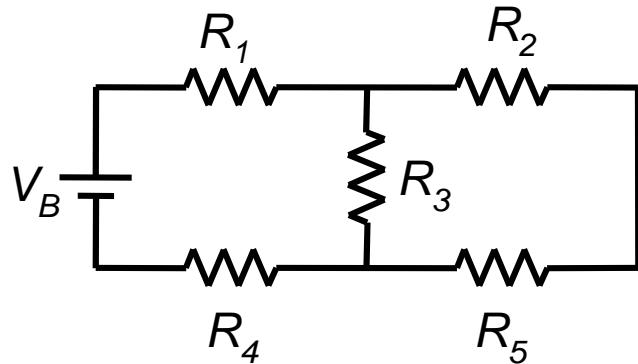Determine the current through each resistor, the total current and the voltage across each resistor.



Note that $V_3 = V_2 + V_5$
and $I_1 = I_3 + I_{25}$.
(within uncertainty)

$$V_B = 24 \text{ V} \quad R_{25} = 126 \Omega$$

$$R_1 = 84 \Omega \quad R_{325} = 54 \Omega$$

$$R_2 = 51 \Omega \quad R_T = 173 \Omega$$

$$R_3 = 96 \Omega$$

$$R_4 = 35 \Omega$$

$$R_5 = 75 \Omega$$

$$I_T = I_1 = I_4 = 0.14 \text{ A}$$

$$I_3 = 0.07 \text{ A}$$

$$I_{25} = I_2 = I_5 = 0.06 \text{ A}$$

$$V_1 = 12 \text{ V}$$

$$V_4 = 5 \text{ V}$$

$$V_{325} = V_3 = V_{25} = 7 \text{ V}$$

$$V_2 = 3 \text{ V}$$

$$V_5 = 5 \text{ V}$$