
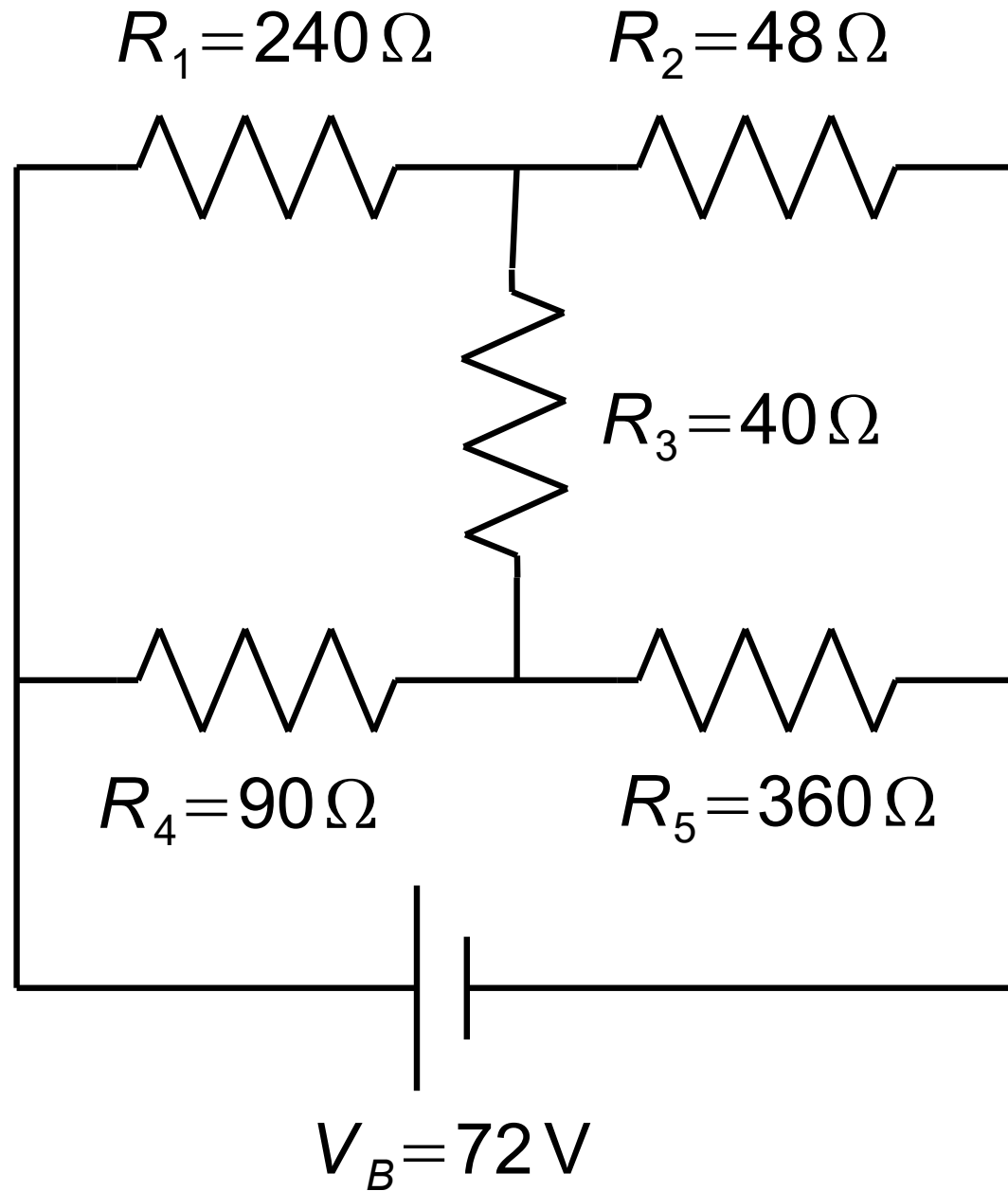


Analyze the given circuit

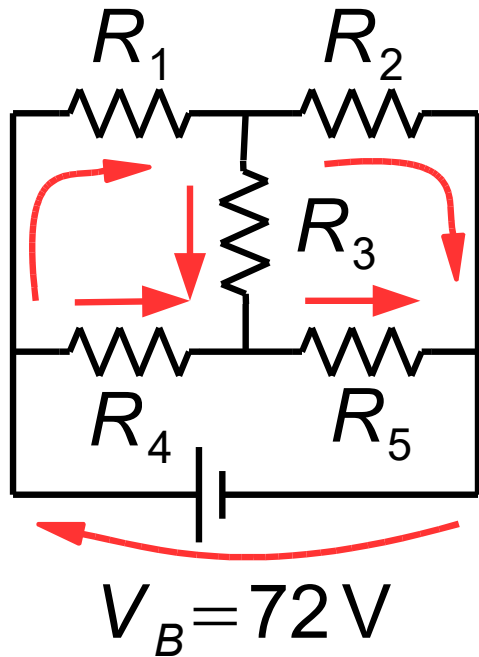



Determine

- the current through each resistor
- the current through the battery
- the potential across each resistor
- the total resistance

$$R_1 = 240\ \Omega$$


$$R_2 = 48\ \Omega$$

$$R_3 = 40\ \Omega$$

$$R_4 = 90\ \Omega$$

$$R_5 = 360\ \Omega$$

Junction Equations

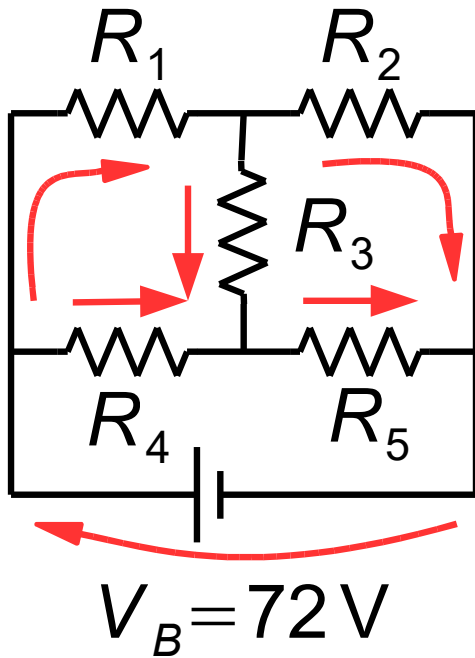

$$I_B = I_1 + I_4$$

$$I_1 = I_2 + I_3$$

$$I_3 + I_4 = I_5$$

$$I_2 + I_5 = I_B$$

$$R_1 = 240\ \Omega$$


$$R_2 = 48\ \Omega$$

$$R_3 = 40\ \Omega$$

$$R_4 = 90\ \Omega$$

$$R_5 = 360\ \Omega$$

Junction Equations

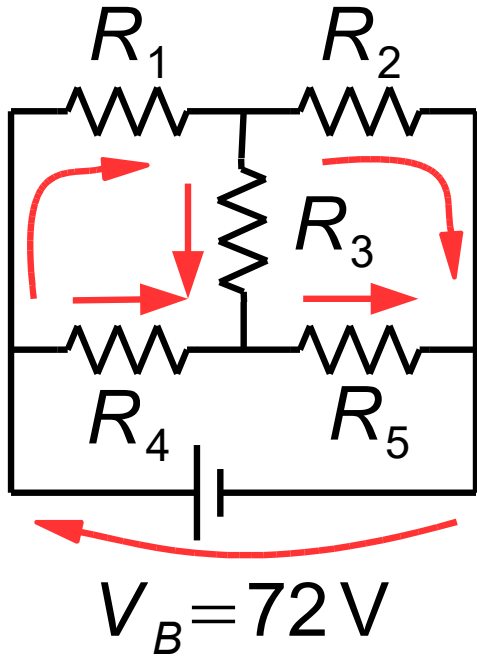

$$I_B = I_1 + I_4$$

$$I_1 = I_2 + I_3$$

$$I_3 + I_4 = I_5$$

$$I_2 + I_5 = I_B$$

Combine

$$I_1 + I_4 = I_2 + I_5$$

$$R_1 = 240\ \Omega$$


$$R_2 = 48\ \Omega$$

$$R_3 = 40\ \Omega$$

$$R_4 = 90\ \Omega$$

$$R_5 = 360\ \Omega$$

Junction Equations

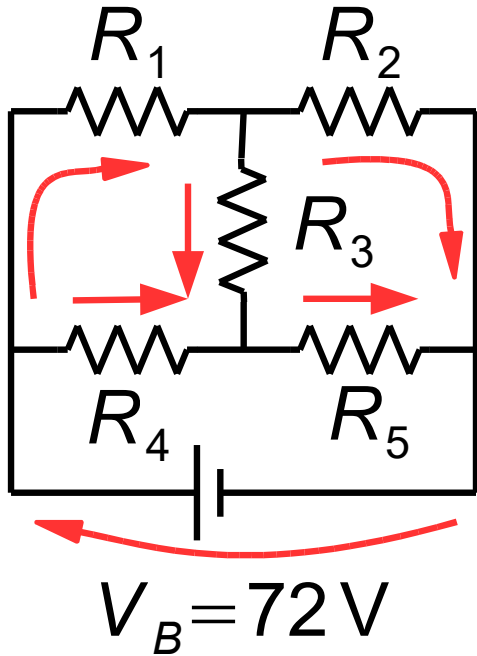

$$R_1 = 240\ \Omega$$
$$R_2 = 48\ \Omega$$
$$R_3 = 40\ \Omega$$
$$R_4 = 90\ \Omega$$
$$R_5 = 360\ \Omega$$

$$I_B = I_1 + I_4$$

$$I_1 = I_2 + I_3$$

$$I_3 + I_4 = I_5$$

$$I_2 + I_5 = I_B$$


Substitute and Simplify

$$I_1 + I_4 = I_2 + I_5$$

$$(I_2 + I_3) + I_4 = I_2 + I_5$$

$$I_3 + I_4 = I_5$$

Junction Equations

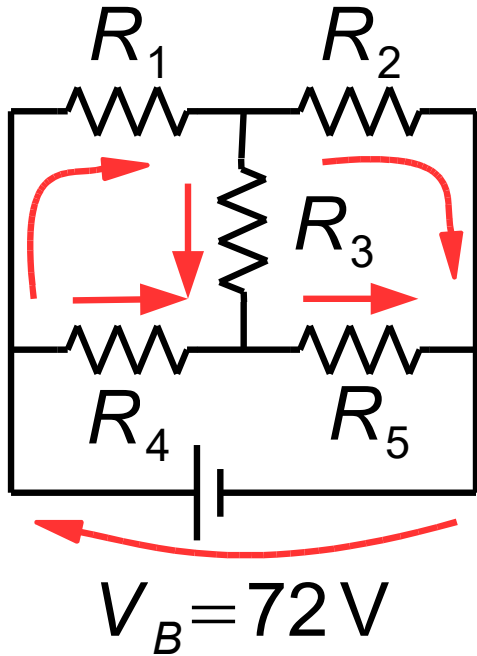

- $R_1 = 240\ \Omega$
- $R_2 = 48\ \Omega$
- $R_3 = 40\ \Omega$
- $R_4 = 90\ \Omega$
- $R_5 = 360\ \Omega$


$$\begin{aligned} I_B &= I_1 + I_4 \\ I_1 &= I_2 + I_3 \\ I_3 + I_4 &= I_5 \\ I_2 + I_5 &= I_B \end{aligned}$$

$$I_1 + I_4 = I_2 + I_5$$

$$(I_2 + I_3) + I_4 = I_2 + I_5$$

$$I_3 + I_4 = I_5$$

Equations are not independent!

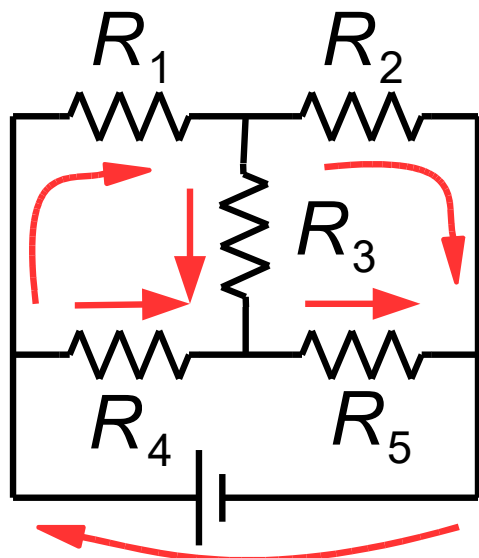

$$V_B = 72 \text{ V}$$

$$R_1 = 240 \, \Omega$$

$$R_2 = 48 \, \Omega$$

$$R_3 = 40 \, \Omega$$

$$R_4 = 90 \, \Omega$$

$$R_5 = 360 \, \Omega$$

$$I_B = I_1 + I_4$$

$$I_1 = I_2 + I_3$$

$$I_2 + I_5 = I_B$$

There are many possible loop equations, but they are not all independent.

Loop Equations

$$- I_1 R_1 - I_3 R_3 + I_4 R_4 = 0$$

$$- I_2 R_2 + I_5 R_5 + I_3 R_3 = 0$$


$$V_B - I_4 R_4 - I_5 R_5 = 0$$

$$V_B - I_1 R_1 - I_2 R_2 = 0$$

$$- I_1 R_1 - I_2 R_2 + I_5 R_5 + I_4 R_4 = 0$$

$$V_B - I_4 R_4 + I_3 R_3 - I_2 R_2 = 0$$
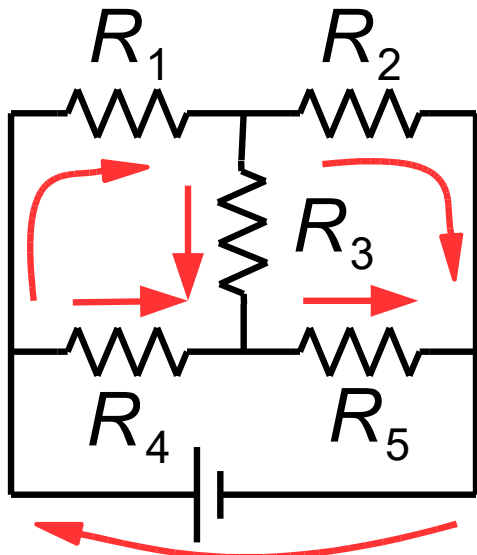
$$V_B - I_1 R_1 - I_3 R_3 - I_5 R_5 = 0$$



$$V_B = 72 \text{ V}$$

$$R_1 = 240 \Omega$$

$$R_2 = 48 \Omega$$

$$R_3 = 40 \Omega$$

$$R_4 = 90 \Omega$$

$$R_5 = 360 \Omega$$

$$I_B = I_1 + I_4$$

$$I_1 = I_2 + I_3$$

$$I_2 + I_5 = I_B$$

Because both I_3 and I_5 only occur in one equation each, I'm guessing these are independent.

Loop Equations

$$-I_1 R_1 - I_3 R_3 + I_4 R_4 = 0$$

$$-I_2 R_2 + I_5 R_5 + I_3 R_3 = 0$$

$$V_B - I_4 R_4 - I_5 R_5 = 0$$


$$V_B - I_1 R_1 - I_2 R_2 = 0$$

$$-I_1 R_1 - I_2 R_2 + I_5 R_5 + I_4 R_4 = 0$$

$$V_B - I_4 R_4 + I_3 R_3 - I_2 R_2 = 0$$

$$V_B - I_1 R_1 - I_3 R_3 - I_5 R_5 = 0$$

Just a little algebra left to do

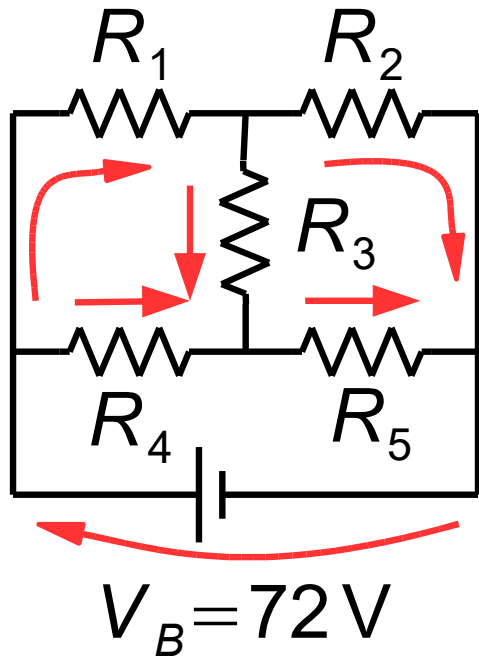

$$I_B = I_1 + I_4$$

$$I_1 = I_2 + I_3$$

$$I_2 + I_5 = I_B$$

$$-I_1 R_1 - I_3 R_3 + I_4 R_4 = 0$$

$$V_B - I_1 R_1 - I_2 R_2 = 0$$

$$-I_1 R_1 - I_2 R_2 + I_5 R_5 + I_4 R_4 = 0$$


$$R_1 = 240\ \Omega$$

$$R_2 = 48\ \Omega$$

$$R_3 = 40\ \Omega$$

$$R_4 = 90\ \Omega$$

$$R_5 = 360\ \Omega$$

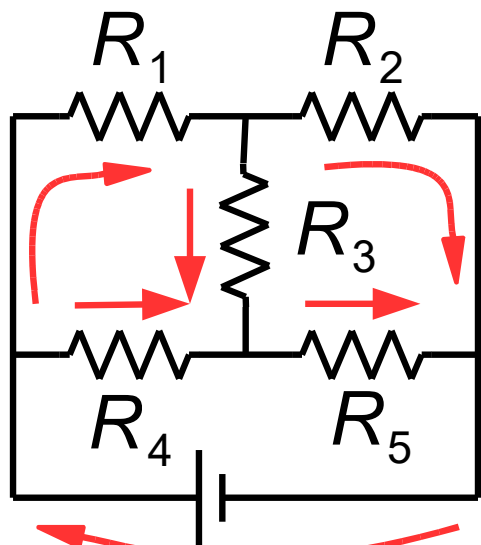

$$V_B = 72 \text{ V}$$

$$R_1 = 240 \Omega$$

$$R_2 = 48 \Omega$$

$$R_3 = 40 \Omega$$

$$R_4 = 90 \Omega$$

$$R_5 = 360 \Omega$$

$$I_B = I_1 + I_4$$

$$I_1 = I_2 + I_3$$

$$I_2 + I_5 = I_B$$


$$-I_1 R_1 - I_3 R_3 + I_4 R_4 = 0$$

$$V_B - I_1 R_1 - I_2 R_2 = 0$$

$$-I_1 R_1 - I_2 R_2 + I_5 R_5 + I_4 R_4 = 0$$

$$I_1 + I_4 = I_2 + I_5$$

Substitute for I_1 everywhere.

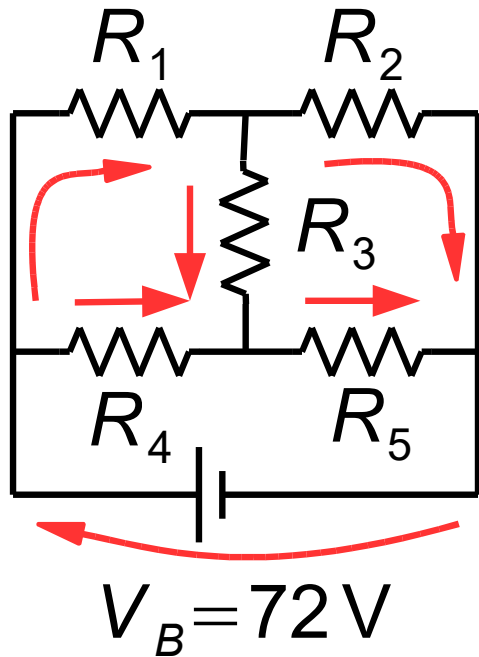

$$I_1 = I_2 + I_3$$

$$I_1 + I_4 = I_2 + I_5$$

$$-I_1 R_1 - I_3 R_3 + I_4 R_4 = 0$$

$$V_B - I_1 R_1 - I_2 R_2 = 0$$

$$-I_1 R_1 - I_2 R_2 + I_5 R_5 + I_4 R_4 = 0$$

$$(I_2 + I_3) + I_4 = I_2 + I_5$$

$$I_3 + I_4 = I_5$$

$$-(I_2 + I_3) R_1 - I_3 R_3 + I_4 R_4 = 0$$

$$-I_2 R_1 - I_3 (R_1 + R_3) + I_4 R_4 = 0$$

$$V_B - (I_2 + I_3) R_1 - I_2 R_2 = 0$$

$$V_B - I_2 (R_1 + R_2) - I_3 R_1 = 0$$

$$-(I_2 + I_3) R_1 - I_2 R_2 + I_5 R_5 + I_4 R_4 = 0$$

$$-I_2 (R_1 + R_2) - I_3 R_1 + I_5 R_5 + I_4 R_4 = 0$$

$$R_1 = 240\ \Omega$$


$$R_2 = 48\ \Omega$$

$$R_3 = 40\ \Omega$$

$$R_4 = 90\ \Omega$$

$$R_5 = 360\ \Omega$$

Substitute for I_5 .

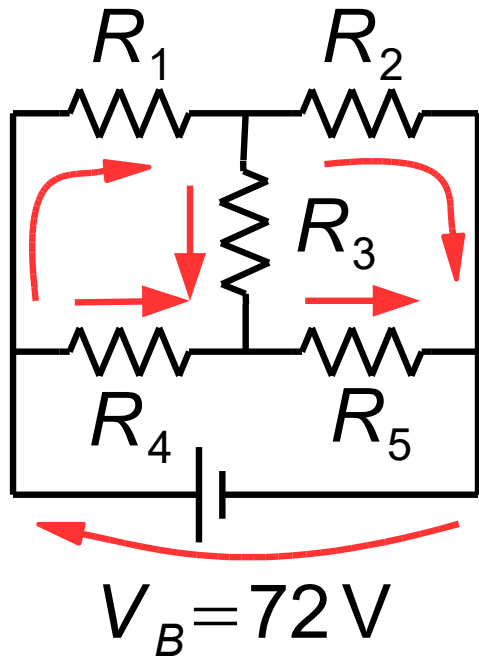

$$I_3 + I_4 = I_5$$

$$\begin{aligned} -I_2 R_1 - I_3(R_1 + R_3) + I_4 R_4 &= 0 \\ V_B - I_2(R_1 + R_2) - I_3 R_1 &= 0 \\ -I_2(R_1 + R_2) - I_3 R_1 + I_5 R_5 + I_4 R_4 &= 0 \end{aligned}$$

$$R_1 = 240\ \Omega$$

$$R_2 = 48\ \Omega$$

$$R_3 = 40\ \Omega$$


$$R_4 = 90\ \Omega$$

$$R_5 = 360\ \Omega$$

$$-I_2(R_1 + R_2) - I_3 R_1 + (I_3 + I_4)R_5 + I_4 R_4 = 0$$

$$-I_2(R_1 + R_2) + I_3(R_5 - R_1) + I_4(R_4 + R_5) = 0$$

Solve for I_3 and substitute.

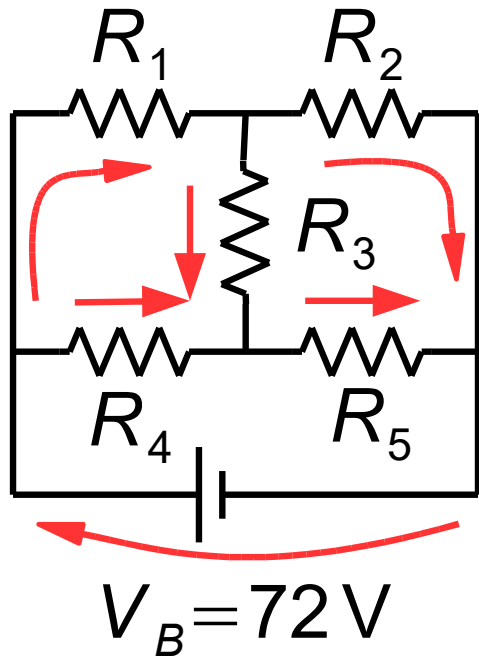

$$\begin{aligned} -I_2 R_1 - I_3 (R_1 + R_3) + I_4 R_4 &= 0 \\ V_B - I_2 (R_1 + R_2) - I_3 R_1 &= 0 \\ -I_2 (R_1 + R_2) + I_3 (R_5 - R_1) + I_4 (R_4 + R_5) &= 0 \end{aligned}$$

It is also acceptable to substitute in the values for the resistances before solving the system of equations.

$$R_1 = 240 \Omega$$


$$R_2 = 48 \Omega$$

$$R_3 = 40 \Omega$$

$$R_4 = 90 \Omega$$

$$R_5 = 360 \Omega$$

Substituting resistance values.

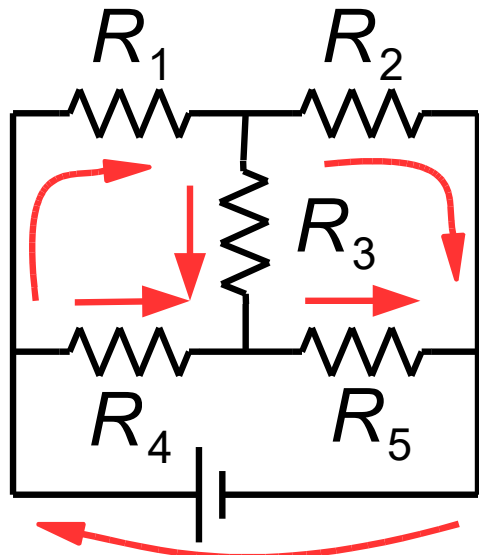

$$V_B = 72 \text{ V}$$

$$R_1 = 240 \Omega$$

$$R_2 = 48 \Omega$$

$$R_3 = 40 \Omega$$

$$R_4 = 90 \Omega$$

$$R_5 = 360 \Omega$$


$$\begin{aligned} -I_2(240 \Omega) - I_3(280 \Omega) + I_4(90 \Omega) &= 0 \\ 72 \text{ V} - I_2(288 \Omega) - I_3(240 \Omega) & \\ -I_2(288 \Omega) + I_3(120 \Omega) + I_4(450 \Omega) &= 0 \end{aligned}$$

Solve for I_3 .

$$\frac{72 \text{ V} - I_2(288 \Omega)}{240 \Omega} = I_3$$

$$0.3 \text{ A} - (1.2)I_2 = I_3$$

Substituting for I_3 .

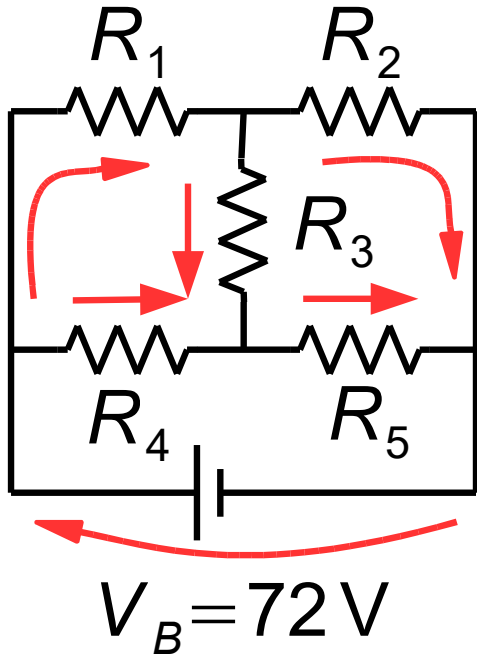

$$R_1 = 240\ \Omega$$

$$R_2 = 48\ \Omega$$

$$R_3 = 40\ \Omega$$

$$R_4 = 90\ \Omega$$


$$R_5 = 360\ \Omega$$

$$\begin{aligned} -I_2(240\ \Omega) - I_3(280\ \Omega) + I_4(90\ \Omega) &= 0 \\ 0.3\text{ A} - (1.2)I_2 &= I_3 \\ -I_2(288\ \Omega) + I_3(120\ \Omega) + I_4(450\ \Omega) &= 0 \end{aligned}$$



$$\begin{aligned} -I_2(240\ \Omega) - [0.3\text{ A} - (1.2)I_2](280\ \Omega) + I_4(90\ \Omega) &= 0 \\ -84\text{ V} + I_2(96\ \Omega) + I_4(90\ \Omega) &= 0 \end{aligned}$$
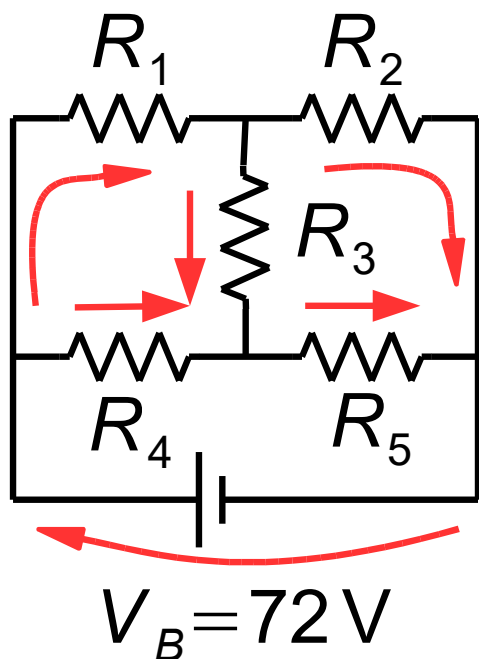
$$\begin{aligned} -I_2(288\ \Omega) + [0.3\text{ A} - (1.2)I_2](120\ \Omega) + I_4(450\ \Omega) &= 0 \\ 36\text{ V} - I_2(432\ \Omega) + I_4(450\ \Omega) &= 0 \end{aligned}$$



$$\begin{aligned}
 -84\text{ V} + I_2(96\ \Omega) + I_4(90\ \Omega) &= 0 \\
 36\text{ V} - I_2(432\ \Omega) + I_4(450\ \Omega) &= 0
 \end{aligned}$$

Solve for I_2 .

$$\frac{36\text{ V} + I_4(450\ \Omega)}{432\ \Omega} = I_2$$

$$0.0833\text{ A} + (1.042)I_4 = I_2$$

Substitute.

$$\begin{aligned}
 -84\text{ V} + [0.0833\text{ A} + (1.042)I_4](96\ \Omega) + I_4(90\ \Omega) &= 0 \\
 -76\text{ V} + I_4(190\ \Omega) &= 0
 \end{aligned}$$

$$0.4\text{ A} = I_4$$


$$R_1 = 240\ \Omega$$

$$R_2 = 48\ \Omega$$

$$R_3 = 40\ \Omega$$

$$R_4 = 90\ \Omega$$

$$R_5 = 360\ \Omega$$

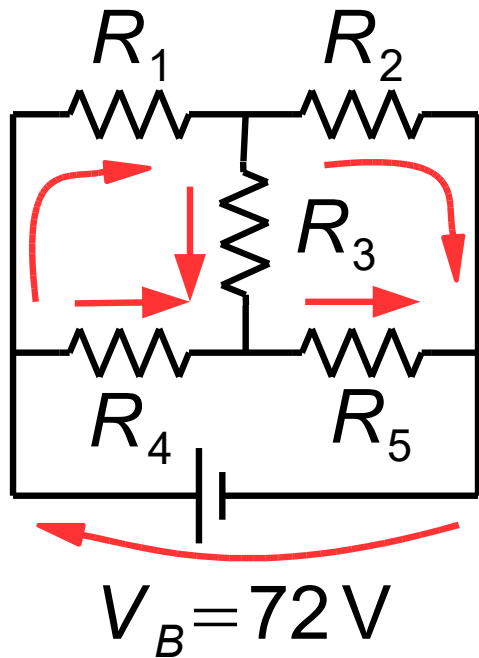

$$0.4\text{ A} = I_4$$

$$0.0833\text{ A} + (1.042)I_4 = I_2$$

$$0.08333\text{ A} + (1.042)(0.4\text{ A}) = I_2$$

$$\boxed{0.5\text{ A} = I_2}$$

$$R_1 = 240\ \Omega$$

$$R_2 = 48\ \Omega$$

$$R_3 = 40\ \Omega$$

$$R_4 = 90\ \Omega$$

$$R_5 = 360\ \Omega$$


$$I_1 = ?$$

$$I_2 = 0.5\text{ A}$$

$$I_3 = ?$$

$$I_4 = 0.4\text{ A}$$

$$I_5 = ?$$

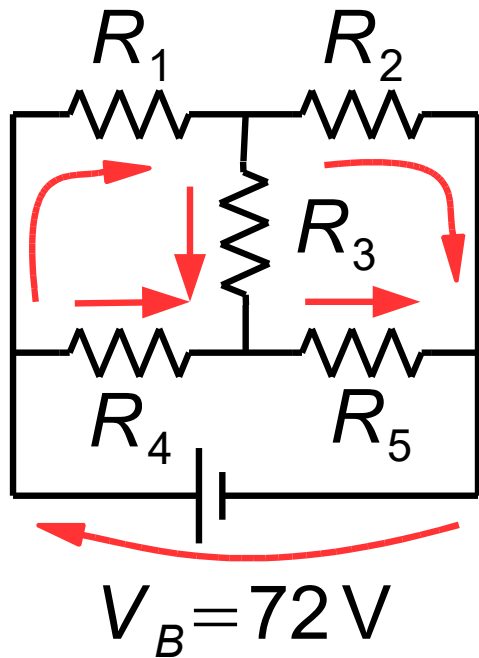

$$0.3\text{ A} - (1.2)I_2 = I_3$$

$$0.3\text{ A} - (1.2)(0.5\text{ A}) = I_3$$

$$\boxed{-0.3\text{ A} = I_3}$$

The negative sign indicates that the direction is opposite to the direction we chose for I_3 .

$$R_1 = 240\ \Omega$$

$$R_2 = 48\ \Omega$$

$$R_3 = 40\ \Omega$$

$$R_4 = 90\ \Omega$$

$$R_5 = 360\ \Omega$$


$$I_1 = ?$$

$$I_2 = 0.5\text{ A}$$

$$I_3 = -0.3\text{ A}$$

$$I_4 = 0.4\text{ A}$$

$$I_5 = ?$$

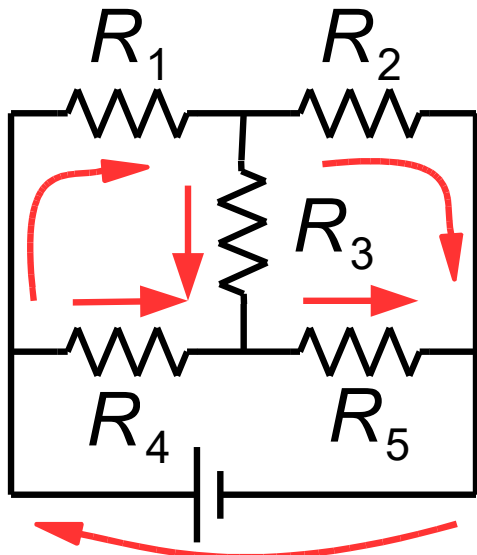

$$V_B = 72\text{ V}$$

$$I_3 + I_4 = I_5$$

$$- 0.3\text{ A} + 0.4\text{ A} = I_5$$

$$0.1\text{ A} = I_5$$

$$R_1 = 240\ \Omega$$

$$R_2 = 48\ \Omega$$

$$R_3 = 40\ \Omega$$

$$R_4 = 90\ \Omega$$

$$R_5 = 360\ \Omega$$


$$I_1 = ?$$

$$I_2 = 0.5\text{ A}$$

$$I_3 = - 0.3\text{ A}$$

$$I_4 = 0.4\text{ A}$$

$$I_5 = 0.1\text{ A}$$

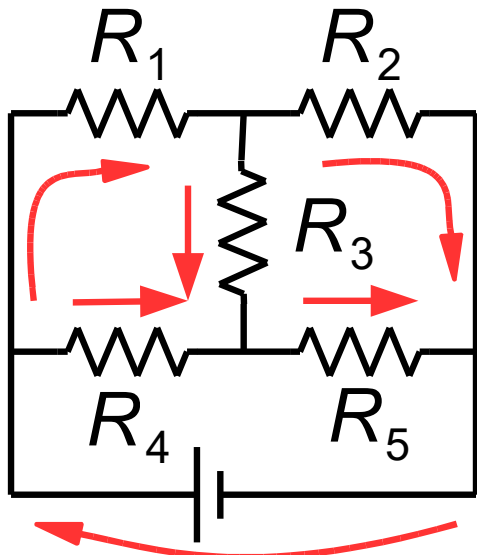

$$V_B = 72\text{ V}$$

$$I_1 = I_2 + I_3$$

$$I_1 = 0.5\text{ A} - 0.3\text{ A}$$

$$I_1 = 0.2\text{ A}$$

$$R_1 = 240\ \Omega$$

$$R_2 = 48\ \Omega$$

$$R_3 = 40\ \Omega$$

$$R_4 = 90\ \Omega$$

$$R_5 = 360\ \Omega$$


$$I_1 = 0.2\text{ A}$$

$$I_2 = 0.5\text{ A}$$

$$I_3 = -0.3\text{ A}$$

$$I_4 = 0.4\text{ A}$$

$$I_5 = 0.1\text{ A}$$

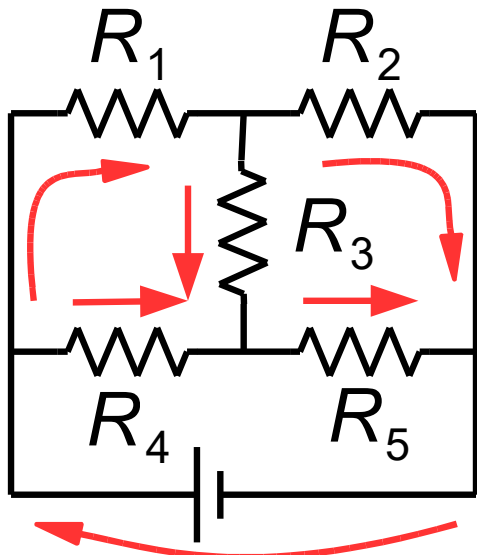

$$V_B = 72\text{ V}$$

$$I_B = I_1 + I_4$$

$$I_B = 0.2\text{ A} + 0.4\text{ A}$$

$$I_B = 0.6\text{ A}$$

$$R_1 = 240\ \Omega$$

$$R_2 = 48\ \Omega$$

$$R_3 = 40\ \Omega$$

$$R_4 = 90\ \Omega$$

$$R_5 = 360\ \Omega$$

$$I_1 = 0.2\text{ A}$$


$$I_2 = 0.5\text{ A}$$

$$I_3 = -0.3\text{ A}$$

$$I_4 = 0.4\text{ A}$$

$$I_5 = 0.1\text{ A}$$

$$I_B = 0.6\text{ A}$$

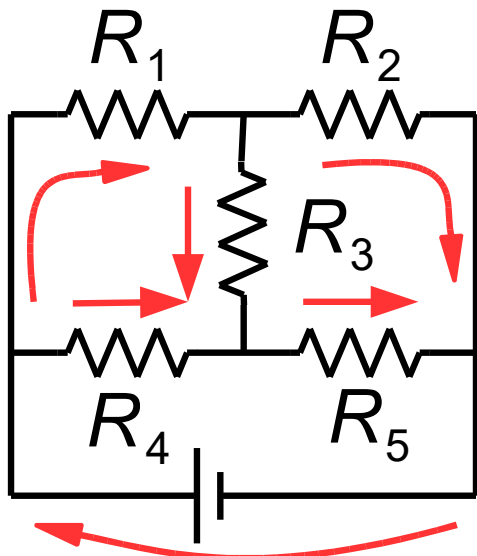

Apply Ohm's Law ... again
... and again ... and ...

$$R_1 = 240 \Omega$$

$$R_2 = 48 \Omega$$

$$R_3 = 40 \Omega$$

$$R_4 = 90 \Omega$$

$$R_5 = 360 \Omega$$

$$R_T = 120 \Omega$$

$$I_1 = 0.2 \text{ A}$$

$$I_2 = 0.5 \text{ A}$$

$$I_3 = -0.3 \text{ A}$$

$$I_4 = 0.4 \text{ A}$$

$$I_5 = 0.1 \text{ A}$$

$$I_B = 0.6 \text{ A}$$

$$V_1 = 48 \text{ V}$$

$$V_2 = 24 \text{ V}$$

$$|V_3| = 12 \text{ V}$$

$$V_4 = 36 \text{ V}$$

$$V_5 = 36 \text{ V}$$

$$V_B = 72 \text{ V}$$