

Resistivity and Resistance

Resistivity, ρ , is a property of a **material** describing the degree to which the material opposes the flow of charges through the material.

Resistance, R , is a property of a **device** describing the degree to which the device opposes the flow of charges through the device.

Power Ratings



Changes as a function of temperature.

$$R = \rho \frac{L}{A} = \rho_0 \frac{L}{A} [1 + \alpha(T - T_0)] = R_0 [1 + \alpha(T - T_0)]$$

$$I = \frac{V}{R} = \frac{V}{\rho \frac{L}{A}} = \frac{V}{\rho_0 \frac{L}{A} [1 + \alpha(T - T_0)]} = \frac{I_0}{1 + \alpha(T - T_0)}$$

$$P = \frac{V^2}{R} = \frac{V^2}{\rho \frac{L}{A}} = \frac{V^2}{\rho_0 \frac{L}{A} [1 + \alpha(T - T_0)]} = \frac{P_0}{1 + \alpha(T - T_0)}$$

Combinations of resistors

Series: 


Parallel: 

Combinations of resistors


Combination of series and parallel:




Neither series nor parallel:

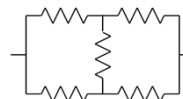







Resistors in Series




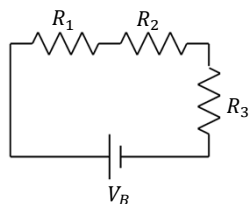


Resistors in Series

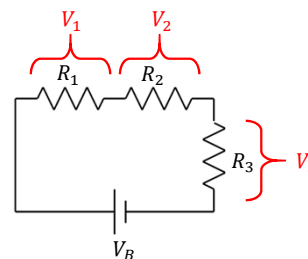

$$V_T = V_1 + V_2 + V_3$$

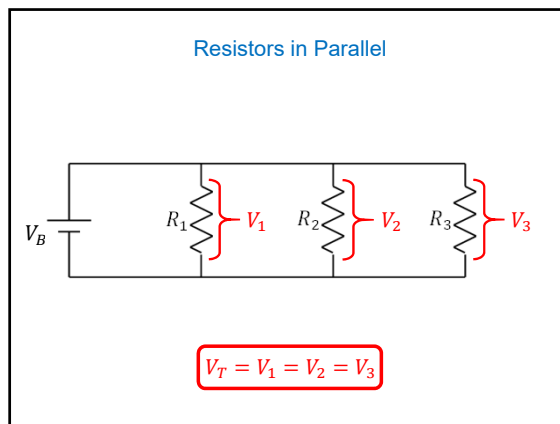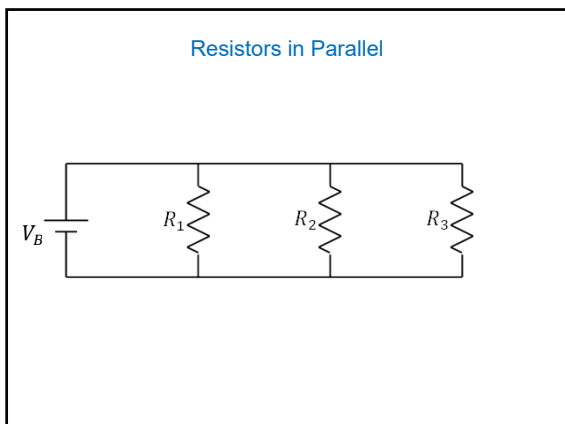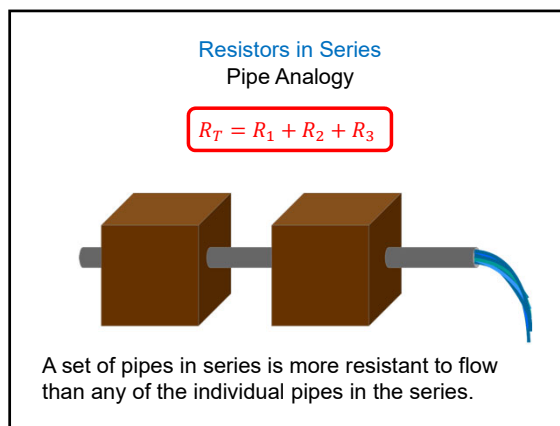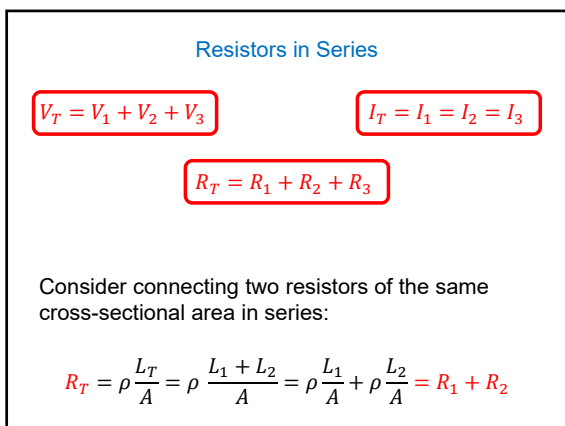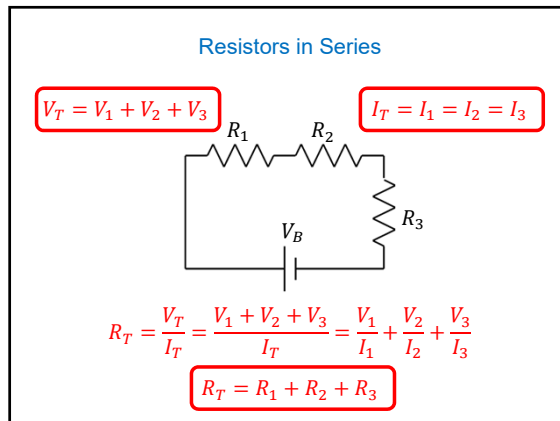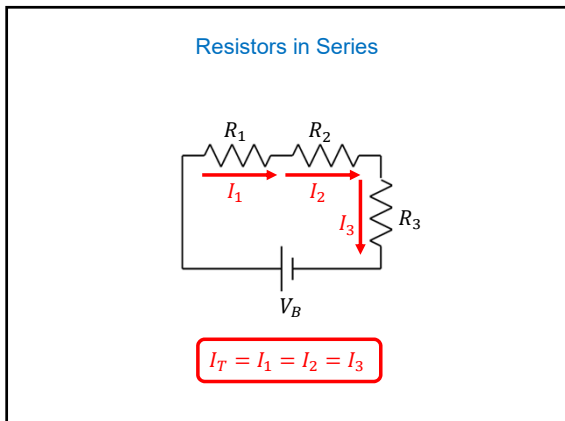

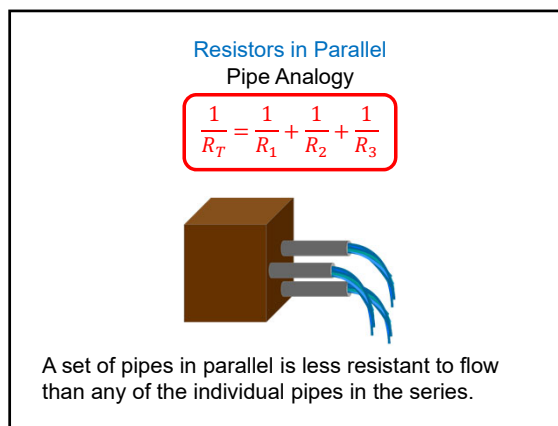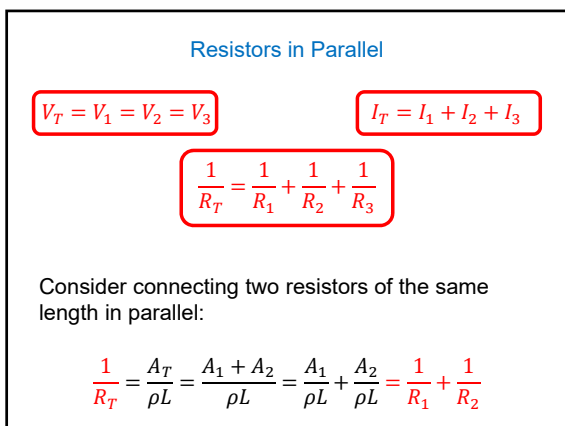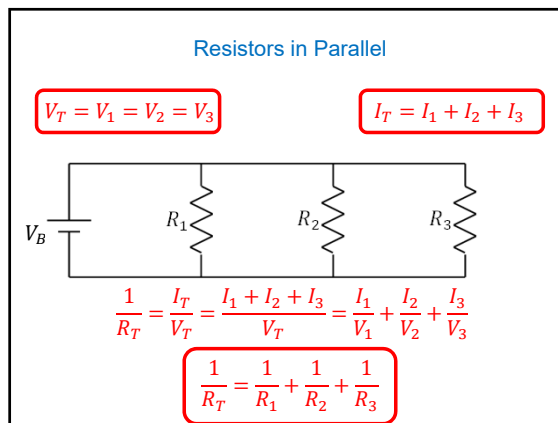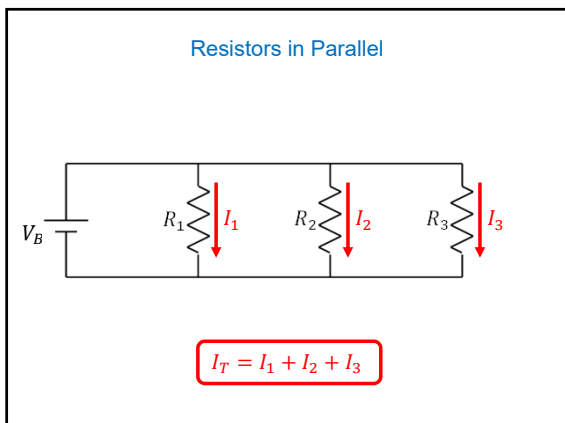

	Series	Parallel
Capacitance	$\frac{1}{C_T} = \sum \frac{1}{C_i}$	$C_T = \sum C_i$
Resistance	$R_T = \sum R_i$	$\frac{1}{R_T} = \sum \frac{1}{R_i}$
Potential Difference	$V_T = \sum V_i$	$V_T = V_i$
Current	$I_T = I_i$	$I_T = \sum I_i$
Charge on Capacitor	$Q_T = Q_i$	$Q_T = \sum Q_i$

OSE's

	Series	Parallel
Capacitance	$\frac{1}{C_T} = \sum \frac{1}{C_i}$	$C_T = \sum C_i$
Resistance	$R_T = \sum R_i$	$\frac{1}{R_T} = \sum \frac{1}{R_i}$
Potential Difference	$V_T = \sum V_i$	$V_T = V_i$
Current	$I_T = I_i$	$I_T = \sum I_i$
Charge on Capacitor	$Q_T = Q_i$	$Q_T = \sum Q_i$


	Series	Parallel
Capacitance	$\frac{1}{C_T} = \sum \frac{1}{C_i}$	$C_T = \sum C_i$
Resistance	$R_T = \sum R_i$	$\frac{1}{R_T} = \sum \frac{1}{R_i}$
Potential Difference	$V_T = \sum V_i$	$V_T = V_i$
Current	$I_T = I_i$	$I_T = \sum I_i$
Charge on Capacitor	$Q_T = Q_i$	$Q_T = \sum Q_i$

Not provided. May be used.

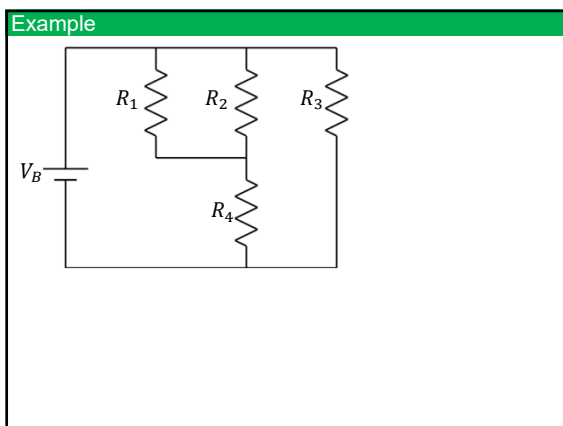Example: Consider the given circuit.

- Determine the total (equivalent) resistance.
- Determine the total current.
- Determine the potential difference across each resistor.
- Determine the current through each resistor.

$R_1 = 60\Omega$
 $R_2 = 40\Omega$
 $R_3 = 75\Omega$
 $R_4 = 26\Omega$
 $V_B = 24V$



Example

$R_1 = 60\Omega$
 $R_2 = 40\Omega$
 $R_3 = 75\Omega$
 $R_4 = 26\Omega$
 $V_B = 24V$


Example

$R_1 = 60\Omega$
 $R_2 = 40\Omega$
 $R_3 = 75\Omega$
 $R_4 = 26\Omega$
 $V_B = 24V$
 $R_{12} = 24\Omega$

Example


$R_1 = 60\Omega$
 $R_2 = 40\Omega$
 $R_3 = 75\Omega$
 $R_4 = 26\Omega$
 $V_B = 24V$
 $R_{12} = 24\Omega$
 $R_{124} = 50\Omega$

Example

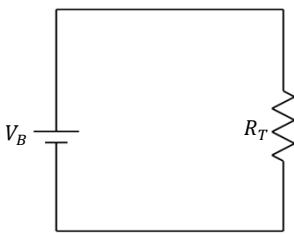


$R_1 = 60\Omega$
 $R_2 = 40\Omega$
 $R_3 = 75\Omega$
 $R_4 = 26\Omega$
 $V_B = 24V$
 $R_{12} = 24\Omega$
 $R_{124} = 50\Omega$
 $R_T = 30\Omega$

Example

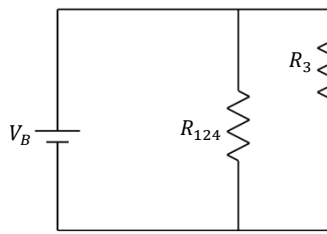


$R_1 = 60\Omega$
 $R_2 = 40\Omega$
 $R_3 = 75\Omega$
 $R_4 = 26\Omega$
 $V_B = 24V$
 $R_{12} = 24\Omega$
 $R_{124} = 50\Omega$
 $R_T = 30\Omega$
 $I_T = 0.8A$

Example

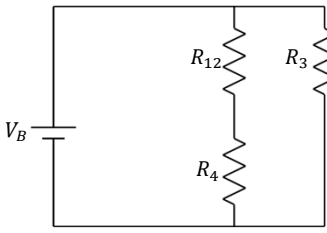

$R_1 = 60\Omega$
 $R_2 = 40\Omega$
 $R_3 = 75\Omega$
 $R_4 = 26\Omega$
 $V_3 = V_{124} = V_B = 24V$
 $R_{12} = 24\Omega$
 $R_{124} = 50\Omega$
 $R_T = 30\Omega$
 $I_T = 0.8A$
 $I_3 = 0.32A$
 $I_{124} = 0.48A$


Example

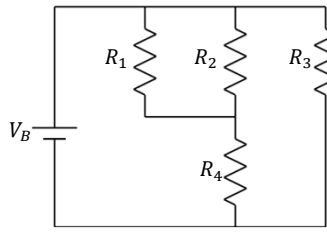

$R_1 = 60\Omega$
 $R_2 = 40\Omega$
 $R_3 = 75\Omega$
 $R_4 = 26\Omega$
 $V_3 = V_{124} = V_B = 24V$
 $R_{12} = 24\Omega$
 $R_{124} = 50\Omega$
 $R_T = 30\Omega$
 $I_T = 0.8A$
 $I_3 = 0.32A$
 $I_{12} = I_4 = I_{124} = 0.48A$
 $V_4 = 12.48V$
 $V_{12} = 11.52V$


Example: Consider the given circuit.

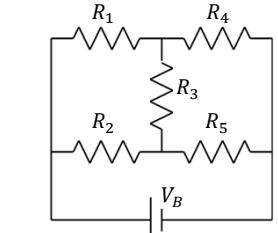(a) Determine the total (equivalent) resistance.
 (b) Determine the total current.
 (b) Determine the potential difference across each resistor.
 (c) Determine the current through each resistor.




$V_B = 50V$
 $R_1 = 30\Omega$
 $R_2 = 90\Omega$
 $R_3 = 40\Omega$
 $R_4 = 52\Omega$
 $R_5 = 20\Omega$

Example:

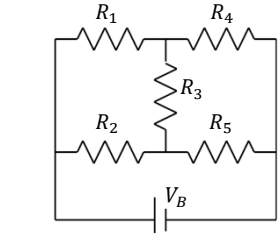


Example:

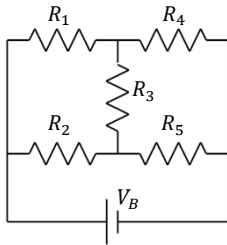


Resistors are neither connected in series nor parallel. Apply Kirchhoff's rules.

- Loop Rule: $\sum \Delta V = 0$
- Junction Rule: $\sum I = 0$ or $\sum I_{in} = \sum I_{out}$

Example:

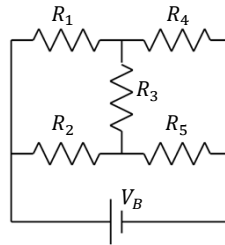

Example:

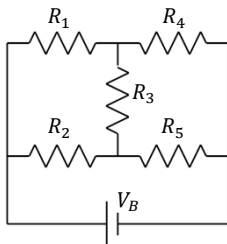

$V_1 = 24V$	$R_1 = 30\Omega$
$V_2 = 36V$	$R_2 = 90\Omega$
$V_3 = 12V$	$R_3 = 40\Omega$
$V_4 = 26V$	$R_4 = 52\Omega$
$V_5 = 14V$	$R_5 = 20\Omega$
$V_B = 50V$	$R_T = 42\Omega$
	$I_1 = 0.8A$
	$I_2 = 0.4A$
	$I_3 = 0.3A$
	$I_4 = 0.5A$
	$I_5 = 0.7A$
	$I_T = 1.2A$