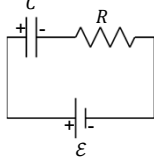


## RC Circuits

What happens when capacitor is connected to a resistor in a circuit?




---

---

---

---

---


---

---

---

## RC Circuits

Apply Kirchoff's loop rule.

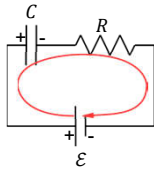

$$\varepsilon - \frac{Q}{C} - IR = 0$$

---

---

---

---

---

---

---

---

## RC Circuits

$$\varepsilon - \frac{Q}{C} - IR = 0$$

$$I = + \frac{dQ}{dt}$$

Positive because current through the resistor is associated with an increase of charge on the capacitor.

$$\varepsilon - \frac{Q}{C} - \frac{dQ}{dt}R = 0$$

---

---

---

---

---

---

---

---

## RC Circuits

$$\varepsilon - \frac{Q}{C} - \frac{dQ}{dt}R = 0$$

$$\varepsilon - \frac{Q}{C} = \frac{dQ}{dt}R$$

$$\frac{\varepsilon C - Q}{RC} = \frac{dQ}{dt}$$

$$\frac{dt}{RC} = \frac{dQ}{\varepsilon C - Q}$$

---

---

---

---

---

---

---

---

## RC Circuits

$$\frac{dt}{RC} = \frac{dQ}{\varepsilon C - Q}$$

$$\int_0^t \frac{dt}{RC} = \int_0^Q \frac{dQ}{\varepsilon C - Q}$$

$$\frac{t}{RC} = -\ln[\varepsilon C - Q]_0^Q$$

$$-\frac{t}{RC} = \ln\left(\frac{\varepsilon C - Q}{\varepsilon C}\right)$$

---

---

---

---

---

---

---

---

## RC Circuits

$$-\frac{t}{RC} = \ln\left(\frac{\varepsilon C - Q}{\varepsilon C}\right)$$

$$e^{-\frac{t}{RC}} = \frac{\varepsilon C - Q}{\varepsilon C}$$

$$\varepsilon C e^{-\frac{t}{RC}} = \varepsilon C - Q$$

$$Q = \varepsilon C(1 - e^{-\frac{t}{RC}})$$

---

---

---

---

---

---

---

---

## RC Circuits

$$-\frac{t}{RC} = \ln\left(\frac{\mathcal{E}C - Q}{\mathcal{E}C}\right)$$

$$e^{-\frac{t}{RC}} = \frac{\mathcal{E}C - Q}{\mathcal{E}C}$$

$$\mathcal{E}C e^{-\frac{t}{RC}} = \mathcal{E}C - Q$$

$$Q = \mathcal{E}C(1 - e^{-\frac{t}{RC}})$$

$$Q = Q_f(1 - e^{-\frac{t}{RC}})$$

---

---

---

---

---

---

---


---

## RC Circuits

## Charging a capacitor

- Charge on capacitor

$$Q = Q_f(1 - e^{-\frac{t}{\tau}})$$

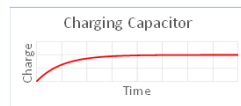

$$(\tau \equiv RC)$$

---

---

---

---

---

---

---

---

## RC Circuits


## Charging a capacitor

- Charge on capacitor

$$Q = Q_f(1 - e^{-\frac{t}{\tau}})$$

- Voltage across capacitor
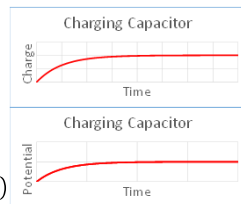
$$V = \frac{Q}{C} = \mathcal{E}(1 - e^{-\frac{t}{\tau}})$$



$$(\tau \equiv RC)$$

---

---

---

---

---

---

---

---

**RC Circuits**




**Charging a capacitor**

- Charge on capacitor  

$$Q = Q_f(1 - e^{-\frac{t}{\tau}})$$
- Voltage across capacitor  

$$V = \frac{Q}{C} = \mathcal{E}(1 - e^{-\frac{t}{\tau}})$$
- Current through resistor  

$$I = \frac{dQ}{dt} = \frac{\mathcal{E}}{R}e^{-\frac{t}{\tau}}$$

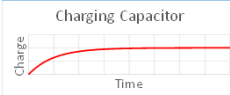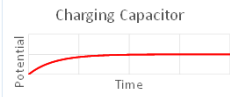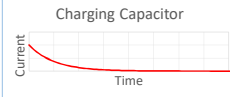---

---

---

---

---


---

---

---

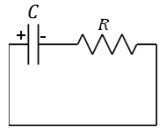**RC Circuits**

What happens when charged capacitor is connected to a resistor in a circuit without a battery?




---

---

---

---

---


---

---

---

**RC Circuits**

Apply Kirchhoff's loop rule.

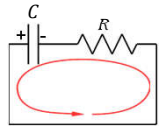

$$\frac{Q}{C} - IR = 0$$


---

---

---

---

---

---

---

---

## RC Circuits

$$\frac{Q}{C} - IR = 0$$

$$I = -\frac{dQ}{dt}$$

Negative because current through the resistor is associated with a decrease of charge on the capacitor.

$$\frac{Q}{C} + \frac{dQ}{dt}R = 0$$

---

---

---

---

---

---

---

---

## RC Circuits

$$\frac{Q}{C} + \frac{dQ}{dt}R = 0$$

$$\frac{dQ}{Q} = -\frac{dt}{RC}$$

$$\ln\left(\frac{Q}{Q_0}\right) = -\frac{t}{RC}$$

$$Q = Q_0 e^{-\frac{t}{RC}}$$

---

---

---

---

---

---

---


---

## RC Circuits

## Discharging a capacitor

- Charge on capacitor

$$Q = Q_0 e^{-\frac{t}{\tau}}$$

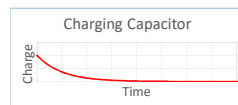

$$(\tau \equiv RC)$$

---

---

---

---

---

---

---

---

RC Circuits



**Discharging a capacitor**

- Charge on capacitor

$$Q = Q_0 e^{-\frac{t}{\tau}}$$

- Voltage across capacitor

$$V = \frac{Q}{C} = \frac{Q_0}{C} e^{-\frac{t}{\tau}}$$

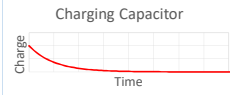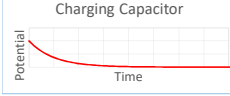( $\tau \equiv RC$ )

---

---

---

---

---

---

---

---

RC Circuits

**Discharging a capacitor**

- Charge on capacitor




$$Q = Q_0 e^{-\frac{t}{\tau}}$$

- Voltage across capacitor

$$V = \frac{Q}{C} = \frac{Q_0}{C} e^{-\frac{t}{\tau}}$$

- Current through resistor

$$I = -\frac{dQ}{dt} = \frac{Q_0}{RC} e^{-\frac{t}{\tau}}$$

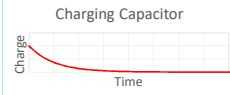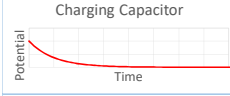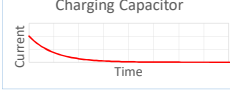---

---

---

---

---

---

---

---

Example: An  $8\mu\text{F}$  capacitor is connected in series with a  $50\Omega$  resistor and a  $60\text{V}$  battery. (a) When does the capacitor become fully charged? (b) What is the charge on the capacitor when it is fully charged?

---

---

---

---

---

---

---

---

Example: An  $8\mu\text{F}$  capacitor is connected in series with a  $50\Omega$  resistor and a  $60\text{V}$  battery. (a) When does the capacitor become fully charged? (b) What is the charge on the capacitor when it is fully charged? (c) When does the capacitor hold a third of its ultimate full charge? (d) What is the current in the resistor when the capacitor holds a third of its ultimate full charge?

---

---

---

---

---

---

---

---