

The gap of square parallel plate capacitor is completely filled by an insulator with dielectric constant  $\kappa$ . The capacitor has sides of length  $a$  and a distance between the plates  $d$ . The isolated capacitor holds charge  $Q$ .

- What is the change in charge on the capacitor?
- The dielectric is removed from the capacitor. What is the change in energy stored on the capacitor?
- What is the change in potential across the capacitor?

1

---

---

---

---

---


---

---

---

The gap of square parallel plate capacitor is completely filled by an insulator with dielectric constant  $\kappa$ . The capacitor has sides of length  $a$  and a distance between the plates  $d$ . The isolated capacitor holds charge  $Q$ .

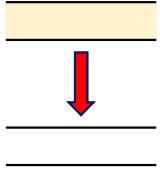- What is the change in charge on the capacitor?
- The dielectric is removed from the capacitor. What is the change in energy stored on the capacitor?
- What is the change in potential across the capacitor?



Let  $C_0$  be without dielectric:  $C_i = \kappa C_0$  and  $C_f = C_0$

$$Q_f = Q_i = Q$$

2

---

---

---

---

---


---

---

---

The gap of square parallel plate capacitor is completely filled by an insulator with dielectric constant  $\kappa$ . The capacitor has sides of length  $a$  and a distance between the plates  $d$ . The isolated capacitor holds charge  $Q$ .

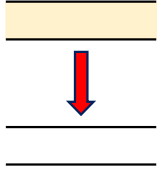- What is the change in charge on the capacitor?
- The dielectric is removed from the capacitor. What is the change in energy stored on the capacitor?
- What is the change in potential across the capacitor?



$$U_i = \frac{1}{2} \frac{Q^2}{C_i} = \frac{1}{2} \frac{Q^2}{\kappa C_0} = \frac{1}{\kappa} \left[ \frac{1}{2} \frac{Q^2}{C_0} \right] = \frac{1}{\kappa} \left[ \frac{1}{2} \frac{Q^2}{C_f} \right] = \frac{1}{\kappa} U_f$$

$$\Delta U = U_f \left( 1 - \frac{1}{\kappa} \right) = \left( \frac{1}{2} \frac{Q^2}{C_0} \right) \left( 1 - \frac{1}{\kappa} \right) = \frac{Q^2 d}{2\epsilon_0 a^2} \left( 1 - \frac{1}{\kappa} \right)$$

3

---

---

---

---

---


---

---

---

The gap of square parallel plate capacitor is completely filled by an insulator with dielectric constant  $\kappa$ . The capacitor has sides of length  $a$  and a distance between the plates  $d$ . The isolated capacitor holds charge  $Q$ .

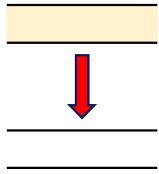- What is the change in charge on the capacitor?
- The dielectric is removed from the capacitor. What is the change in energy stored on the capacitor?
- What is the change in potential across the capacitor?



$$V_i = \frac{Q_i}{C_i} = \frac{Q_f}{\kappa C_0} = \frac{1}{\kappa} \left( \frac{Q_f}{C_0} \right) = \frac{1}{\kappa} \left( \frac{Q_f}{C_f} \right) = \frac{1}{\kappa} V_f$$

$$\Delta V = \left( 1 - \frac{1}{\kappa} \right) V_f = \left( 1 - \frac{1}{\kappa} \right) \left( \frac{Q_f}{C_0} \right) = \left( 1 - \frac{1}{\kappa} \right) \left( \frac{Qd}{\epsilon_0 a^2} \right)$$

4

---

---

---

---

---

---

---

---

A cylindrical wire has a diameter  $d$  and length  $L$  and is made of a metal with a conductivity  $\sigma$  at temperature  $T_0$ .

- What is the resistance of the wire?
- What is the resistance of the wire at temperature  $T$  if the temperature coefficient of resistivity is  $\alpha$ ?

5

---

---

---

---

---

---

---

---

A cylindrical wire has a diameter  $d$  and length  $L$  and is made of a metal with a conductivity  $\sigma$  at temperature  $T_0$ .

- What is the resistance of the wire?
- What is the resistance of the wire at temperature  $T$  if the temperature coefficient of resistivity is  $\alpha$ ?

$$R = \rho \frac{L}{A} = \frac{1}{\sigma} \frac{L}{\pi \left( \frac{d}{2} \right)^2} = \frac{4L}{\sigma \pi d^2}$$

6

---

---

---

---

---

---

---

---

A cylindrical wire has a diameter  $d$  and length  $L$  and is made of a metal with a conductivity  $\sigma$  at temperature  $T_0$ .

- What is the resistance of the wire?
- What is the resistance of the wire at temperature  $T$  if the temperature coefficient of resistivity is  $\alpha$ ?

$$R = \rho \frac{L}{A} = \frac{1}{\sigma} \frac{L}{\pi \left(\frac{d}{2}\right)^2} = \frac{4L}{\sigma \pi d^2}$$

$$R = \rho \frac{L}{A} = \rho_0 [1 + \alpha(T - T_0)] \frac{L}{A} = R_0 [1 + \alpha(T - T_0)] = \frac{4L}{\sigma \pi d^2} [1 + \alpha(T - T_0)]$$

7

---

---

---

---

---

---

---

---

A wire of radius  $r$  and length  $L$  is connected across a potential difference  $\Delta V$ . The wire is made of a material with free electron density  $n$ .

- What is the current in the wire?
- What is the drift velocity of the free electrons in the wire?

8

---

---

---

---

---

---

---

---

A wire of radius  $r$  and length  $L$  is connected across a potential difference  $\Delta V$ . The wire is made of a material with free electron density  $n$  and resistivity  $\rho$ .

- What is the current in the wire?
- What is the drift velocity of the free electrons in the wire?

$$I = JA = \sigma EA = \frac{1}{\rho} \frac{\Delta V}{L} A = \frac{\Delta V \pi r^2}{\rho L} \quad \text{OR} \quad I = \frac{\Delta V}{R} = \frac{\Delta V \pi r^2}{\rho L}$$

9

---

---

---

---

---

---

---

---

A wire of radius  $r$  and length  $L$  is connected across a potential difference  $\Delta V$ . The wire is made of a material with free electron density  $n$  and resistivity  $\rho$ .

- What is the current in the wire?
- What is the drift velocity of the free electrons in the wire?

$$I = JA = \sigma EA = \frac{1}{\rho} \frac{\Delta V}{L} A = \frac{\Delta V \pi r^2}{\rho L} \quad \text{OR} \quad I = \frac{\Delta V}{R} = \frac{\Delta V \pi r^2}{\rho L}$$

$$v_d = \frac{J}{ne} = \frac{\sigma E}{ne} = \frac{E}{\rho ne} = \frac{\Delta V}{\rho neL}$$

10

---

---

---

---

---


---

---

---

Consider the given circuit.

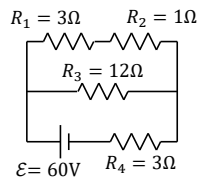- What is the equivalent resistance for the circuit?
- What is the current through  $R_3$ ?
- What is the power dissipated by  $R_2$ ?



11

---

---

---

---

---


---

---

---

Consider the given circuit.

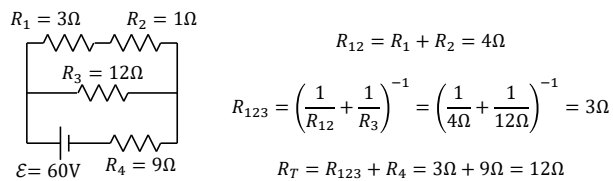- What is the equivalent resistance for the circuit?
- What is the current through  $R_3$ ?
- What is the power dissipated by  $R_2$ ?



12

---

---

---

---

---


---

---

---

Consider the given circuit.

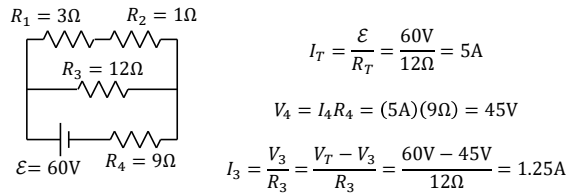- What is the equivalent resistance for the circuit?
- What is the current through  $R_3$ ?
- What is the power dissipated by  $R_2$ ?



13

---

---

---

---

---


---

---

---

Consider the given circuit.

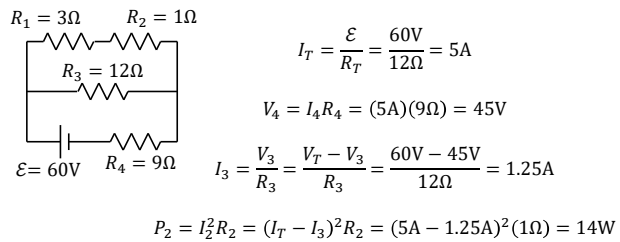- What is the equivalent resistance for the circuit?
- What is the current through  $R_3$ ?
- What is the power dissipated by  $R_2$ ?



14

---

---

---

---

---


---

---

---

A 12V battery with an internal resistance  $r = 0.5\Omega$  is connected to a resistor with resistance  $R = 5.5\Omega$ .

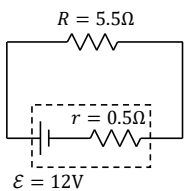- What is the current in the circuit?
- What is the terminal voltage across the battery?
- What is the rate at which chemical energy is converted to electrical energy in the battery?



15

---

---

---

---

---


---

---

---

A 12V battery with an internal resistance  $r = 0.5\Omega$  is connected to a resistor with resistance  $R = 5.5\Omega$ .

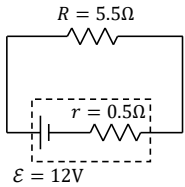- What is the current in the circuit?
- What is the terminal voltage across the battery?
- What is the rate at which chemical energy is converted to electrical energy in the battery?



$$I = \frac{\mathcal{E}}{R + r} = \frac{12\text{V}}{5.5\Omega + 0.5\Omega} = \frac{12\text{V}}{6\Omega} = 2\text{A}$$

16

---

---

---

---

---


---

---

---

A 12V battery with an internal resistance  $r = 0.5\Omega$  is connected to a resistor with resistance  $R = 5.5\Omega$ .

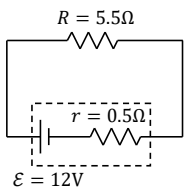- What is the current in the circuit?
- What is the terminal voltage across the battery?
- What is the rate at which chemical energy is converted to electrical energy in the battery?



$$I = \frac{\mathcal{E}}{R + r} = \frac{12\text{V}}{5.5\Omega + 0.5\Omega} = \frac{12\text{V}}{6\Omega} = 2\text{A}$$

$$V_{\text{terminal}} = \mathcal{E} - Ir = 12\text{V} - (2\text{A})(0.5\Omega) = 11\text{V}$$

17

---

---

---

---

---


---

---

---

A 12V battery with an internal resistance  $r = 0.5\Omega$  is connected to a resistor with resistance  $R = 5.5\Omega$ .

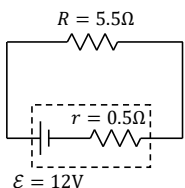- What is the current in the circuit?
- What is the terminal voltage across the battery?
- What is the rate at which chemical energy is converted to electrical energy in the battery?



$$I = \frac{\mathcal{E}}{R + r} = \frac{12\text{V}}{5.5\Omega + 0.5\Omega} = \frac{12\text{V}}{6\Omega} = 2\text{A}$$

$$V_{\text{terminal}} = \mathcal{E} - Ir = 12\text{V} - (2\text{A})(0.5\Omega) = 11\text{V}$$

$$P_{\mathcal{E}} = I\mathcal{E} = (2\text{A})(12\text{V}) = 24\text{W}$$

18

---

---

---

---

---


---

---

---

A pair of galvanometers are used to make a voltmeter and an ammeter. They have an internal resistance  $r_G$  and experience full deflection with a current  $I_G$ .

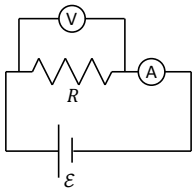- What resistance should be used for the series resistor in the voltmeter to get full deflection for a voltage  $V_{\max}$ ?
- What resistance should be used for the shunt resistor in the ammeter to get full deflection for a current  $I_{\max}$ ?



19

---

---

---

---

---



---

---

---

A pair of galvanometers are used to make a voltmeter and an ammeter. They have an internal resistance  $r_G$  and experience full deflection with a current  $I_G$ .

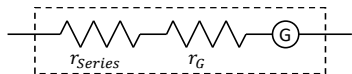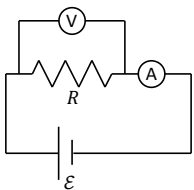- What resistance should be used for the series resistor in the voltmeter to get full deflection for a voltage  $V_{\max}$ ?
- What resistance should be used for the shunt resistor in the ammeter to get full deflection for a current  $I_{\max}$ ?



$$V_{\max} = I_G (r_{\text{Series}} + r_G)$$

$$r_{\text{Series}} = \frac{V_{\max}}{I_G} - r_G$$

20

---

---

---

---

---


---

---

---


A pair of galvanometers are used to make a voltmeter and an ammeter. They have an internal resistance  $r_G$  and experience full deflection with a current  $I_G$ .

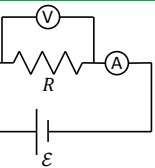- What resistance should be used for the series resistor in the voltmeter to get full deflection for a voltage  $V_{\max}$ ?
- What resistance should be used for the shunt resistor in the ammeter to get full deflection for a current  $I_{\max}$ ?



$$I_G r_G = (I_{\max} - I_G) r_{\text{Shunt}}$$
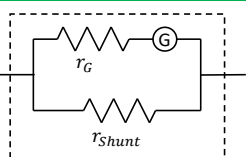
$$\frac{I_G}{I_{\max} - I_G} r_G = r_{\text{Shunt}}$$



21

---

---

---

---

---

---

---

---

A capacitor with capacitance  $C$  is connected in series with a resistor with resistance  $R$  and a battery with emf  $\mathcal{E}$ .

- What is the charge on the capacitor at time  $t$ ?
- When is the charge on the capacitor 60% of its final charge?
- What is the current through the resistor at time  $t$ ?
- What is the voltage across the resistor when the voltage across the capacitor is  $V_C$ ?

22

---

---

---

---

---

---

---

---

A capacitor with capacitance  $C$  is connected in series with a resistor with resistance  $R$  and a battery with emf  $\mathcal{E}$ .

- What is the charge on the capacitor at time  $t$ ?
- When is the charge on the capacitor 60% of its final charge?
- What is the current through the resistor at time  $t$ ?
- What is the voltage across the resistor when the voltage across the capacitor is  $V_C$ ?

$$Q = Q_f (1 - e^{-t/RC})$$

$$Q = C\mathcal{E} (1 - e^{-t/RC})$$

23

---

---

---

---

---

---

---

---

A capacitor with capacitance  $C$  is connected in series with a resistor with resistance  $R$  and a battery with emf  $\mathcal{E}$ .

- What is the charge on the capacitor at time  $t$ ?
- When is the charge on the capacitor 60% of its final charge?
- What is the current through the resistor at time  $t$ ?
- What is the voltage across the resistor when the voltage across the capacitor is  $V_C$ ?

$$0.6Q_f = Q_f (1 - e^{-t/RC})$$

$$e^{-t/RC} = 0.4$$

$$t = -RC \ln(0.4)$$

24

---

---

---

---

---

---

---

---



A capacitor with capacitance  $C$  is connected in series with a resistor with resistance  $R$  and a battery with emf  $\mathcal{E}$ .

- What is the charge on the capacitor at time  $t$ ?
- When is the charge on the capacitor 60% of its final charge?
- What is the current through the resistor at time  $t$ ?
- What is the voltage across the resistor when the voltage across the capacitor is  $V_C$ ?

$$I = \frac{dQ}{dt} = \frac{d}{dt} [\mathcal{E}C (1 - e^{-t/RC})]$$

$$I = \frac{\mathcal{E}}{R} e^{-t/RC}$$

25

---

---

---

---

---

---

---

---

A capacitor with capacitance  $C$  is connected in series with a resistor with resistance  $R$  and a battery with emf  $\mathcal{E}$ .

- What is the charge on the capacitor at time  $t$ ?
- When is the charge on the capacitor 60% of its final charge?
- What is the current through the resistor at time  $t$ ?
- What is the voltage across the resistor when the voltage across the capacitor is  $V_C$ ?

$$0 = \mathcal{E} - V_C - V_R$$

$$V_R = \mathcal{E} - V_C$$

26

---

---

---

---

---

---

---

---

A particle with mass  $m$ , charge  $q$  and velocity  $v_0 \hat{i}$  enters a region with uniform magnetic field  $B_0 \hat{j}$ .

- What is the radius of the particle's trajectory?
- What is the rotational direction of the particle?

27

---

---

---

---

---

---

---

---

A particle with mass  $m$ , charge  $q$  and velocity  $v_0\hat{i}$  enters a region with uniform magnetic field  $B_0\hat{j}$ .

- What is the radius of the particle's trajectory?
- What is the rotational direction of the particle?

$$\frac{mv^2}{r} = |q\vec{v} \times \vec{B}|$$

$$\frac{mv^2}{r} = qvB$$

$$\frac{mv}{qB} = r$$



28

---

---

---

---

---


---

---

---

A uniform magnetic field  $\vec{B} = B_x\hat{i} + B_y\hat{j}$  exists in a region. Consider the flux through a rectangle of sides  $a$  and  $b$ .

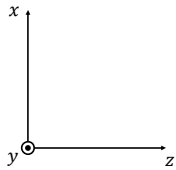- The rectangle is in the  $xy$ -plane.
- The rectangle is in the  $yz$ -plane.



29

---

---

---

---

---


---

---

---

A uniform magnetic field  $B_0\hat{k}$  exists in a region with the given current arrangement.

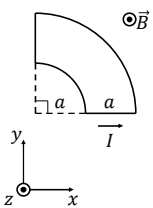- What is the force on the straight sections of wire?
- What is the force on the arced sections of wire?



30

---

---

---

---

---


---

---

---

A uniform magnetic field  $B_0\hat{k}$  exists in a region with the given current arrangement.  $\vec{F} = I\vec{L} \times \vec{B}$

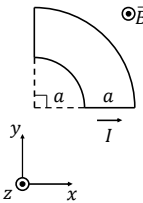- What is the force on the straight sections of wire?
- What is the force on the arced sections of wire?



Bottom:  $\vec{F}_{bottom} = Ia\hat{i} \times B_0\hat{k}$   
 $\vec{F}_{bottom} = -IaB_0\hat{j}$

Left:  $\vec{F}_{left} = Ia(-\hat{j}) \times B_0\hat{k}$   
 $\vec{F}_{left} = -IaB_0\hat{i}$

31

---

---

---

---

---


---

---

---

A uniform magnetic field  $B_0\hat{k}$  exists in a region with the given current arrangement.  $\vec{F} = I\vec{L} \times \vec{B}$

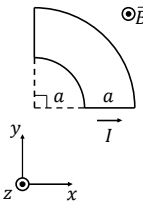- What is the force on the straight sections of wire?
- What is the force on the arced sections of wire?



Upper Arc:  $\vec{F}_{ua} = \int_0^{\pi/2} I2ad\phi(-\sin\phi\hat{i} + \cos\phi\hat{j}) \times B_0\hat{k}$   
 $\vec{F}_{ua} = 2IaB_0 \int_0^{\pi/2} d\phi(\sin\phi\hat{j} + \cos\phi\hat{i})$   
 $\vec{F}_{ua} = 2IaB_0[-\cos\phi\hat{j} + \sin\phi\hat{i}]_0^{\pi/2}$   
 $\vec{F}_{ua} = 2IaB_0(\hat{i} + \hat{j})$

32

---

---

---

---

---


---

---

---

A uniform magnetic field  $B_0\hat{k}$  exists in a region with the given current arrangement.  $\vec{F} = I\vec{L} \times \vec{B}$

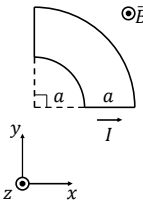- What is the force on the straight sections of wire?
- What is the force on the arced sections of wire?



Lower Arc:  $\vec{F}_{la} = \int_0^{\pi/2} Iad\phi(\sin\phi\hat{i} - \cos\phi\hat{j}) \times B_0\hat{k}$   
 $\vec{F}_{la} = IaB_0 \int_0^{\pi/2} d\phi(-\sin\phi\hat{j} - \cos\phi\hat{i})$   
 $\vec{F}_{la} = IaB_0[\cos\phi\hat{j} - \sin\phi\hat{i}]_0^{\pi/2}$   
 $\vec{F}_{la} = -IaB_0(\hat{i} + \hat{j})$

33

---

---

---

---

---

---

---


---

A uniform magnetic field  $B_0\hat{k}$  exists in a region with the given current arrangement.

- What is the force on the straight sections of wire?
- What is the force on the arced sections of wire?

$$\vec{F} = I\vec{L} \times \vec{B}$$
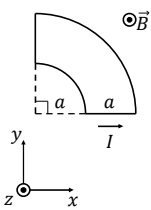
$$\vec{F} = \int Id\vec{s} \times \vec{B}$$



$$\left. \begin{aligned} \vec{F}_{bottom} &= -IaB_0\hat{j} \\ \vec{F}_{left} &= -IaB_0\hat{i} \\ \vec{F}_{ua} &= 2IaB_0(\hat{i} + \hat{j}) \\ \vec{F}_{la} &= -IaB_0(\hat{i} + \hat{j}) \end{aligned} \right\} \rightarrow \vec{F}_{Total} = 0$$

34

---

---

---

---

---

---

---

---

A coil of wire with  $N$  turns and a radius  $R$  lies in the  $xy$ -plane and carries a current  $I$ . There is a uniform magnetic field  $\vec{B} = B_x\hat{i} + B_z\hat{k}$ .

- What is the energy of the dipole?
- What is the torque on the dipole?

35

---

---

---

---

---

---

---

---

A coil of wire with  $N$  turns and a radius  $R$  lies in the  $xy$ -plane and carries a current  $I$  such that  $\vec{A}$  is in the positive  $z$ -direction. There is a uniform magnetic field  $\vec{B} = B_x\hat{i} + B_z\hat{k}$ .

- What is the energy of the dipole?
- What is the torque on the dipole?

$$\begin{aligned} U &= -\vec{\mu} \cdot \vec{B} & \vec{\tau} &= \vec{\mu} \times \vec{B} \\ U &= -NI\vec{A} \cdot \vec{B} & \vec{\tau} &= NI\vec{A}\hat{k} \times (B_x\hat{i} + B_z\hat{k}) \\ U &= -NI\pi R^2 B_z & \vec{\tau} &= NIAB_x\hat{j} \end{aligned}$$

36

---

---

---

---

---

---

---

---