

Phys 208 – Homework (HW10) – SP13 (Due Monday, February 18, 2013)

Problems: 2.16.6(b), 2.16.7(a), 2.16.8, 2.16.9, 2.16.10

Answers: 2.16.7(a) Series:  $1 + 2i$  Parallel:  $3(3 - i)/5$

$$2.16.9(a) \quad \omega = \frac{R}{2L} + \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}} \quad (b) \quad \omega = 1/\sqrt{LC}$$

HW10.1 In an R-L-C series circuit, the source has a constant voltage amplitude of 50 V and an angular frequency  $\omega = 1000$  rad/sec.  $R = 300 \Omega$ ,  $L = 0.9$  H, and  $C = 2.0 \mu\text{F}$ .

- a) What is the impedance of the circuit?    b) What is the current amplitude?
- c) What are the voltage amplitudes across the resistor, inductor, and capacitor?
- d) Determine the current phase angle  $\phi$ . Does the current lead or lag the applied voltage?
- e) What power is consumed in the circuit?
- f) Determine the resonant angular frequency of the circuit.
- g) What is the current amplitude at resonance?
- h) What power is consumed in the circuit at resonance?

Answers: HW11.1 (a)  $Z = 300 \Omega + i 400 \Omega$     (b) 0.1 A

(c)  $V_R = 30$  V,  $V_L = 90$  V,  $V_C = 50$  V

(d) Phase angle equals 53.1 degrees. Current lags the voltage.

(e) 1.5 W    (f) 745 rad/sec    (g) 0.167 A    (h) 4.17 W

Phys 208 – Homework (HW11) – SP13 (Due Wednesday, February 20, 2013)

HW 11.1 An AC-circuit consists of a resistor and capacitor in series. The source has a voltage amplitude of 50 V and an angular frequency  $\omega = 1000$  rad/s.  $R = 300 \Omega$  and  $C = 2 \mu\text{F}$ .

- a) What is the magnitude of the impedance of the circuit?
- b) What is the current amplitude?

- c) What are the voltage amplitudes across the resistor and across the capacitor?
- d) What is the phase angle  $\phi$ ? Does the current lag or lead the source voltage?
- e) Determine the power consumed in the circuit.
- f) Construct the phasor diagram.

HW 11.2 A  $100\ \Omega$  resistor, a  $0.1\ \mu\text{F}$  capacitor, and a  $0.1\ \text{H}$  inductor are connected in parallel to a voltage source with amplitude  $100\ \text{V}$ .

- a) What is the resonant angular frequency?
- b) What is the maximum total current through the parallel combination at resonance?
- c) What is the maximum current in the resistor, inductor, and capacitor at resonance?

HW 11.3 A circuit draws  $330\ \text{W}$  from a  $110\ \text{V}$ ,  $60\ \text{Hz}$  AC-line. The power factor is  $0.6$  and the current lags the voltage. Note: The  $110\ \text{V}$  is the  $V_{\text{rms}}$  (or root-mean-square voltage) of the line.

- a) Find the capacitance of the series capacitor that will result in a power factor of unity.
- b) What power will then be drawn from the power line?

Answers: HW 11.1 a)  $583\ \Omega$  b)  $0.0858\ \text{A}$  c)  $25.7\ \text{V}$ ,  $42.9\ \text{V}$  d)  $59^\circ$ , leads e)  $1.10\ \text{W}$

HW 11.2 a)  $\omega_0 = 10^4\ \text{rad/s}$  b)  $1\ \text{A}$  c)  $1\ \text{A}$ ,  $0.1\ \text{A}$ ,  $-0.1\ \text{A}$

HW 11.3 a)  $151\ \mu\text{F}$  b)  $917\ \text{W}$

Read the following: Ch 4-Sect 11 Change of variables  
 Ch 4-Sect 12 Differentiation of integrals; Leibniz' Rule  
 Ch 5- Sect 4 Change of variables in integrals; Jacobians

Problems: Ch 4 – 4.11.1, 4.11.6, 4.11.7

Test 1 Friday, February 22, 2013